

# OPAMP

Operational Amplifier, also called as an Op-Amp, is an integrated circuit, which can be used to perform various linear, non-linear, and mathematical operations. An op-amp is a **direct coupled high gain amplifier**. You can operate op-amp both with AC and DC signals. This chapter discusses the characteristics and types of op-amps.

## Construction of Operational Amplifier

An op-amp consists of differential amplifier(s), a level translator and an output stage. A differential amplifier is present at the input stage of an op-amp and hence an op-amp consists of **two input terminals**. One of those terminals is called as the **inverting terminal** and the other one is called as the **non-inverting terminal**. The terminals are named based on the phase relationship between their respective inputs and outputs.

## Characteristics of Operational Amplifier

The important characteristics or parameters of an operational amplifier are as follows –

- Open loop voltage gain
- Output offset voltage
- Common Mode Rejection Ratio
- Slew Rate

This section discusses these characteristics in detail as given below –

### Open loop voltage gain

The open loop voltage gain of an op-amp is its differential gain without any feedback path.

Mathematically, the open loop voltage gain of an op-amp is represented as –

$$A_v = \frac{v_0}{v_1 - v_2}$$

$$A_v = v_0 / v_1 - v_2$$

### Output offset voltage

The voltage present at the output of an op-amp when its differential input voltage is zero is called as **output offset voltage**.

### Common Mode Rejection Ratio

Common Mode Rejection Ratio (**CMRR**) of an op-amp is defined as the ratio of the closed loop differential gain,  $A_d$  and the common mode gain,  $A_c$ .

Mathematically, CMRR can be represented as –

$$CMRR = \frac{A_d}{A_c}$$

$$CMRR = A_d / A_c$$

Note that the common mode gain,  $A_c$  of an op-amp is the ratio of the common mode output voltage and the common mode input voltage.

## Slew Rate

Slew rate of an op-amp is defined as the maximum rate of change of the output voltage due to a step input voltage.

Mathematically, slew rate (SR) can be represented as –

$$SR = \text{Maximum of } \frac{dV_0}{dt}$$

$$SR = \text{Maximum of } dV_0/dt$$

Where,  $V_0$  is the output voltage. In general, slew rate is measured in either  $V/\mu\text{Sec}$  or  $V/\text{mSec}$ .

## Types of Operational Amplifiers


An op-amp is represented with a triangle symbol having two inputs and one output.

Op-amps are of two types: **Ideal Op-Amp** and **Practical Op-Amp**.

They are discussed in detail as given below –
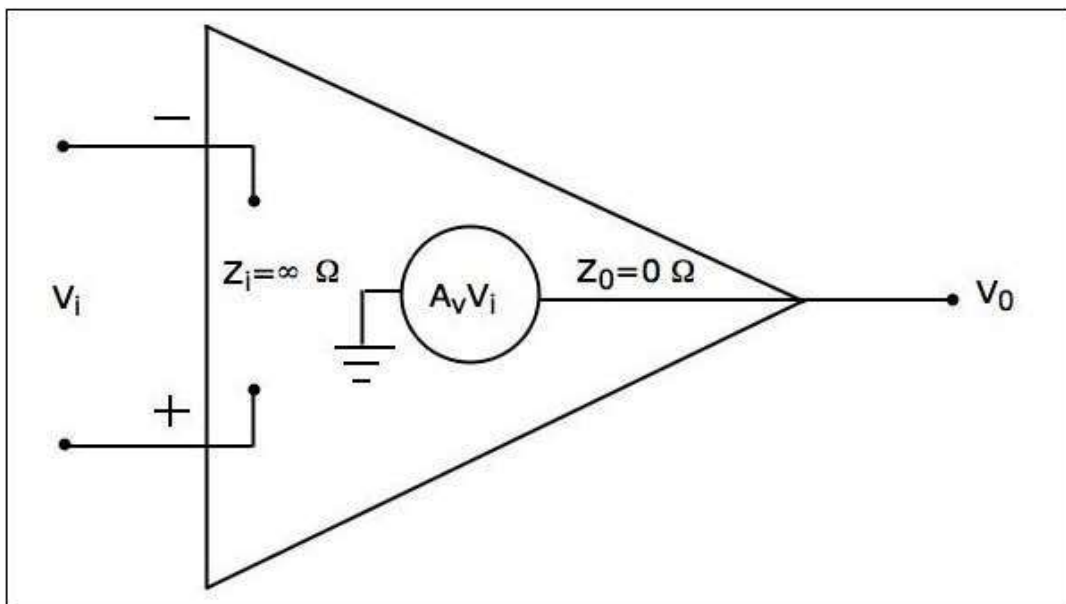
### Ideal Op-Amp

An ideal op-amp exists only in theory, and does not exist practically. The **equivalent circuit** of an ideal op-amp is shown in the figure given below –



An **ideal op-amp** exhibits the following characteristics –

Input impedance  $Z_i = \infty \Omega$   $Z_i = \infty \Omega$

Output impedance  $Z_o = 0 \Omega$   $Z_o = 0 \Omega$

Open loop voltage gain  $A_v = \infty$   $A_v = \infty$

If (the differential) input voltage  $V_i = 0V$   $V_i = 0V$ , then the output voltage will be

$V_o = 0V$   $V_o = 0V$


Bandwidth is **infinity**. It means, an ideal op-amp will amplify the signals of any frequency without any attenuation.

Common Mode Rejection Ratio (**CMRR**) is **infinity**.

Slew Rate (**SR**) is **infinity**. It means, the ideal op-amp will produce a change in the output instantly in response to an input step voltage.
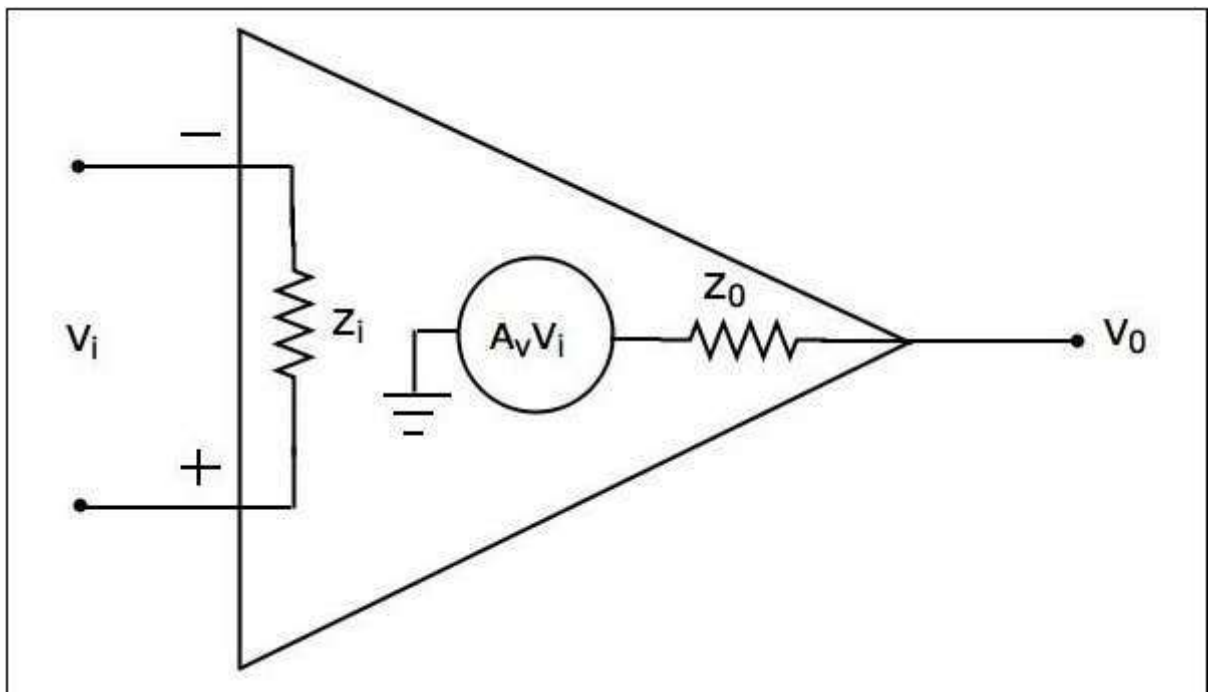
## Practical Op-Amp

Practically, op-amps are not ideal and deviate from their ideal characteristics because of some imperfections during manufacturing. The **equivalent circuit** of a practical op-amp is shown in the following figure –



A **practical op-amp** exhibits the following characteristics –

Input impedance,  $Z_i$   $Z_i$  in the order of **Mega ohms**.

Output impedance,  $Z_o$   $Z_o$  in the order of **few ohms**..

Open loop voltage gain,  $A_v$   $A_v$  will be **high**.

When you choose a practical op-amp, you should check whether it satisfies the following conditions –

Input impedance,  $Z_i$   $Z_i$  should be as high as possible.

Output impedance,  $Z_o$   $Z_o$  should be as low as possible.

Open loop voltage gain,  $A_v$   $A_v$  should be as high as possible.

Output offset voltage should be as low as possible.

The operating Bandwidth should be as high as possible.

CMRR should be as high as possible.

Slew rate should be as high as possible.

**Note** – IC 741 op-amp is the most popular and practical op-amp.

# Op-Amp-Applications

A circuit is said to be **linear**, if there exists a linear relationship between its input and the output. Similarly, a circuit is said to be **non-linear**, if there exists a non-linear relationship between its input and output.

Op-amps can be used in both linear and non-linear applications. The following are the basic applications of op-amp –

- Inverting Amplifier

- Non-inverting Amplifier


- Voltage follower

This chapter discusses these basic applications in detail.
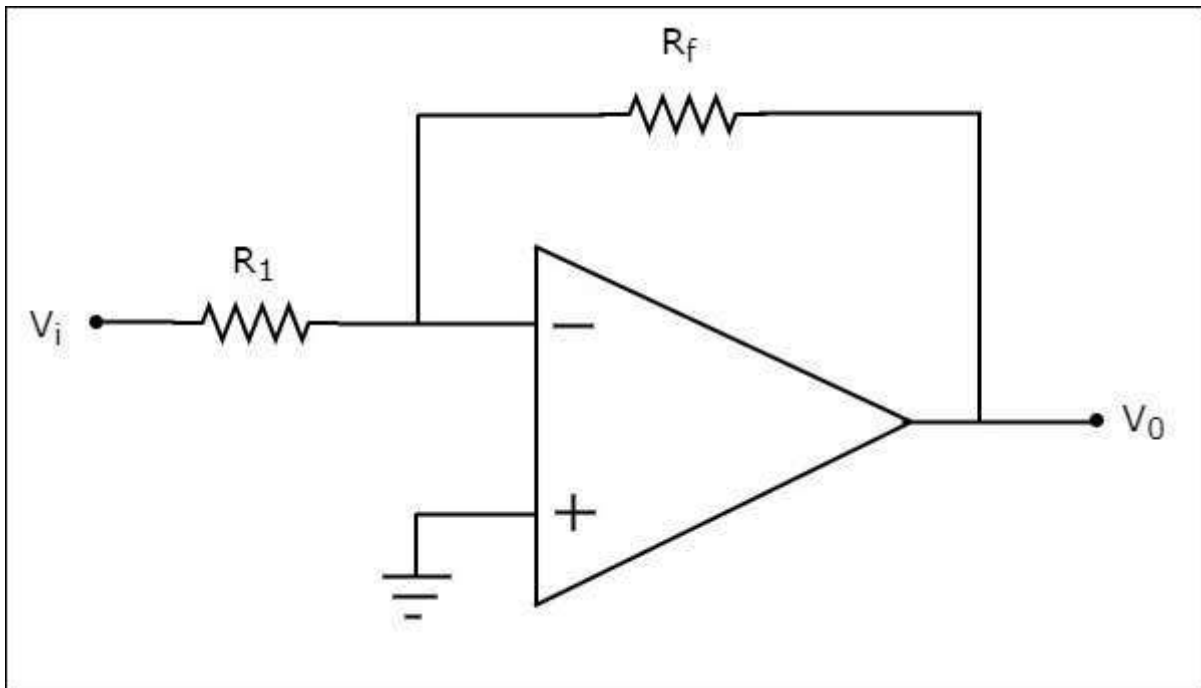
## Inverting Amplifier

An inverting amplifier takes the input through its inverting terminal through a resistor  $R_1$ , and produces its amplified version as the output. This amplifier not only amplifies the input but also inverts it (changes its sign).

The **circuit diagram** of an inverting amplifier is shown in the following figure –



Note that for an op-amp, the voltage at the inverting input terminal is equal to the voltage at its non-inverting input terminal. Physically, there is no short between those two terminals but **virtually**, they are in **short** with each other.

In the circuit shown above, the non-inverting input terminal is connected to ground. That means zero volts is applied at the non-inverting input terminal of the op-amp.

According to the **virtual short concept**, the voltage at the inverting input terminal of an op-amp will be zero volts.

The **nodal equation** at this terminal's node is as shown below –

$$\frac{0 - V_i}{R_1} + \frac{0 - V_0}{R_f} = 0$$

$$0 - V_i R_1 + 0 - V_0 R_f = 0$$

$$\Rightarrow \frac{-V_i}{R_1} = \frac{V_0}{R_f}$$

$$\Rightarrow -V_i R_1 = V_0 R_f$$

$$\Rightarrow V_0 = \left( \frac{-R_f}{R_1} \right) V_i$$

$$\Rightarrow V_0 = (-R_f R_1) V_i$$

$$\Rightarrow \frac{V_0}{V_i} = \frac{-R_f}{R_1}$$

$$\Rightarrow V_0 V_i = -R_f R_1$$


The ratio of the output voltage  $V_0$  and the input voltage  $V_i$  is the voltage-gain or gain of the amplifier. Therefore, the **gain of inverting amplifier** is equal to  $-\frac{R_f}{R_1}$ .

Note that the gain of the inverting amplifier is having a **negative sign**. It indicates that there exists a  $180^\circ$  phase difference between the input and the output.
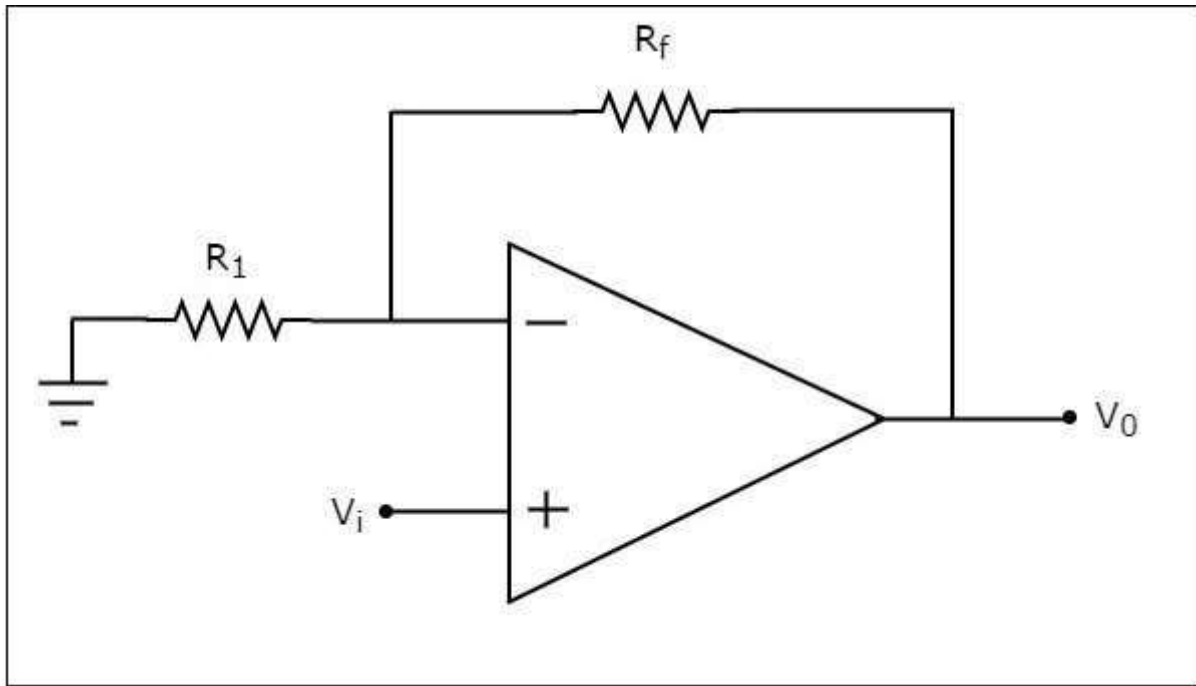
## Non-Inverting Amplifier

A non-inverting amplifier takes the input through its non-inverting terminal, and produces its amplified version as the output. As the name suggests, this amplifier just amplifies the input, without inverting or changing the sign of the output.

The **circuit diagram** of a non-inverting amplifier is shown in the following figure –



In the above circuit, the input voltage  $V_i$  is directly applied to the non-inverting input terminal of op-amp. So, the voltage at the non-inverting input terminal of the op-amp will be  $V_i$ .

By using **voltage division principle**, we can calculate the voltage at the inverting input terminal of the op-amp as shown below –

$$\Rightarrow V_1 = V_0 \left( \frac{R_1}{R_1 + R_f} \right)$$

$$\Rightarrow V_1 = V_0 \left( \frac{R_1}{R_1 + R_f} \right)$$

According to the **virtual short concept**, the voltage at the inverting input terminal of an op-amp is same as that of the voltage at its non-inverting input terminal.

$$\Rightarrow V_1 = V_i$$

$$\Rightarrow V_1 = V_i$$

$$\Rightarrow V_0 \left( \frac{R_1}{R_1 + R_f} \right) = V_i$$

$$\Rightarrow V_0 \left( \frac{R_1}{R_1 + R_f} \right) = V_i$$

$$\Rightarrow \frac{V_0}{V_i} = \frac{R_1 + R_f}{R_1}$$

$$\Rightarrow V_0 V_i = R_1 + R_f R_1$$

$$\Rightarrow \frac{V_0}{V_i} = 1 + \frac{R_f}{R_1}$$

$$\Rightarrow V_0 V_i = 1 + R_f R_1$$


Now, the ratio of output voltage  $V_0$  and input voltage  $V_i$  or the voltage-gain or **gain of the non-inverting amplifier** is equal to  $1 + \frac{R_f}{R_1}$ .

Note that the gain of the non-inverting amplifier is having a **positive sign**. It indicates that there is no phase difference between the input and the output.
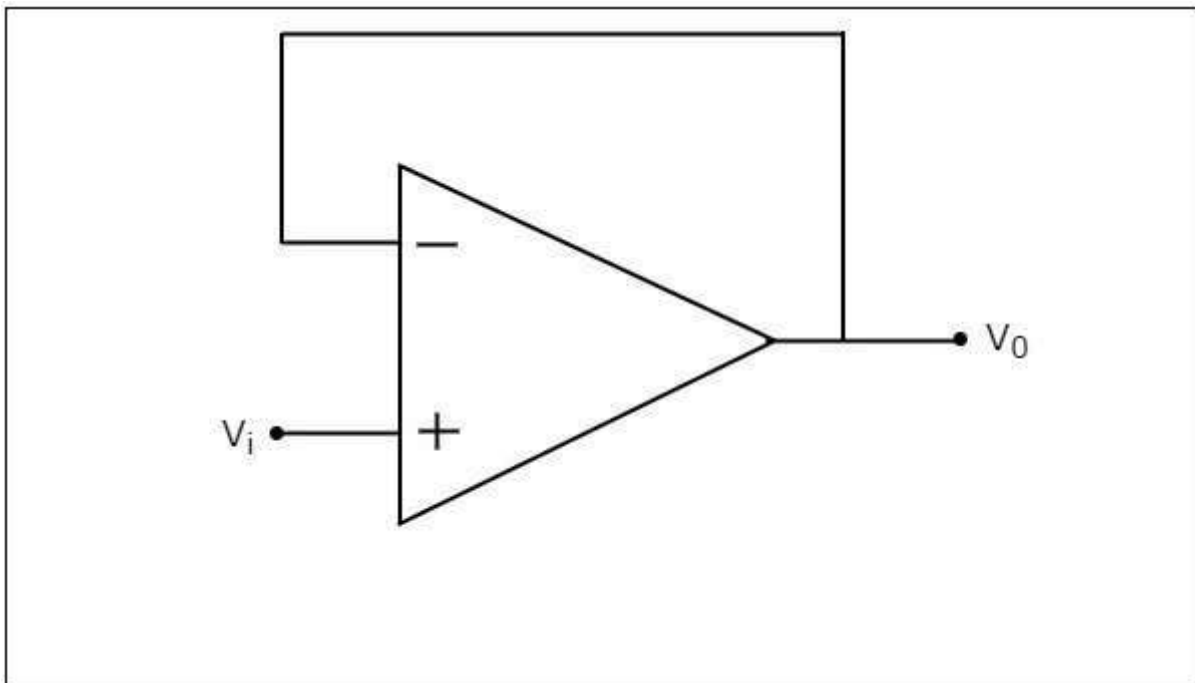
## Voltage follower

A **voltage follower** is an electronic circuit, which produces an output that follows the input voltage. It is a special case of non-inverting amplifier.

If we consider the value of feedback resistor,  $R_f$  as zero ohms and (or) the value of resistor,  $R_1$  as infinity ohms, then a non-inverting amplifier becomes a voltage follower. The **circuit diagram** of a voltage follower is shown in the following figure –



In the above circuit, the input voltage  $V_i$  is directly applied to the non-inverting input terminal of the op-amp. So, the voltage at the non-inverting input terminal of op-amp is equal to  $V_i$ . Here, the output is



directly connected to the inverting input terminal of opamp. Hence, the voltage at the inverting input terminal of op-amp is equal to  $V_0$ .

According to the **virtual short concept**, the voltage at the inverting input terminal of the op-amp is same as that of the voltage at its non-inverting input terminal.

$$\Rightarrow V_0 = V_i$$

$$\Rightarrow V_0 = V_i$$

So, the output voltage  $V_0$  of a voltage follower is equal to its input voltage  $V_i$ .

Thus, the **gain of a voltage follower** is equal to one since, both output voltage  $V_0$  and input voltage

$V_i$  of voltage follower are same.

## Arithmetic Circuits

In the previous chapter, we discussed about the basic applications of op-amp. Note that they come under the linear operations of an op-amp. In this chapter, let us discuss about arithmetic circuits, which are also linear applications of op-amp.


The electronic circuits, which perform arithmetic operations are called as **arithmetic circuits**. Using op-amps, you can build basic arithmetic circuits such as an **adder** and a **subtractor**. In this chapter, you will learn about each of them in detail.

### Adder

An adder is an electronic circuit that produces an output, which is equal to the sum of the applied inputs. This section discusses about the op-amp based adder circuit.

An op-amp based adder produces an output equal to the sum of the input voltages applied at its inverting terminal. It is also called as a **summing amplifier**, since the output is an amplified one.

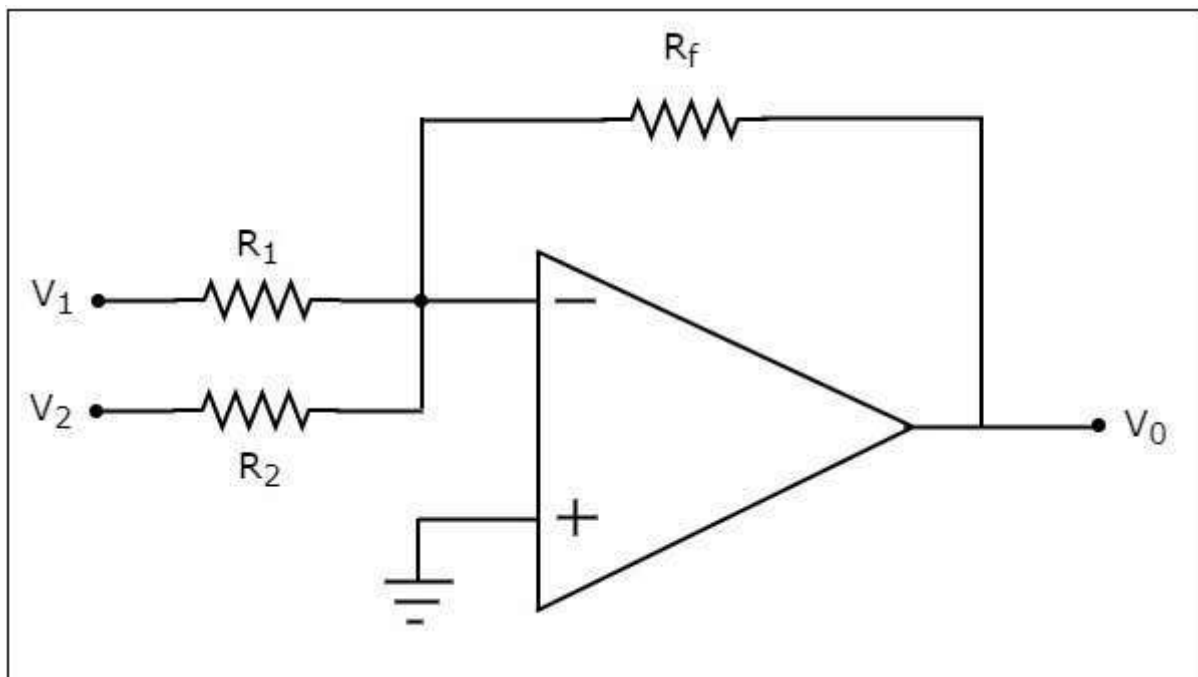The **circuit diagram** of an op-amp based adder is shown in the following figure –



In the above circuit, the non-inverting input terminal of the op-amp is connected to ground. That means zero volts is applied at its non-inverting input terminal.

According to the **virtual short concept**, the voltage at the inverting input terminal of an op-amp is same as that of the voltage at its non-inverting input terminal. So, the voltage at the inverting input terminal of the op-amp will be zero volts.

The **nodal equation** at the inverting input terminal's node is

$$\frac{0 - V_1}{R_1} + \frac{0 - V_2}{R_2} + \frac{0 - V_0}{R_f} = 0$$

$$0 - V_1 R_1 + 0 - V_2 R_2 + 0 - V_0 R_f = 0$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{V_0}{R_f}$$

$$\Rightarrow V_1 R_1 + V_2 R_2 = V_0 R_f$$

$$\Rightarrow V_0 = R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$\Rightarrow V_0 = R_f (V_1 R_1 + V_2 R_2)$$

If  $R_f = R_1 = R_2 = R$   $R_f = R_1 = R_2 = R$ , then the output voltage  $V_0$  will be –

$$V_0 = -R \left( \frac{V_1}{R} + \frac{V_2}{R} \right)$$

$$V_0 = -(V_1 + V_2)$$

$$\Rightarrow V_0 = -(V_1 + V_2)$$

$$\Rightarrow V_0 = -(V_1 + V_2)$$

Therefore, the op-amp based adder circuit discussed above will produce the sum of the two input voltages  $V_1$  and  $V_2$ , as the output, when all the resistors present in the circuit are of same value. Note that


the output voltage  $V_0$  of an adder circuit is having a **negative sign**, which indicates that there exists a  $180^\circ$  phase difference between the input and the output.

## Subtractor

A subtractor is an electronic circuit that produces an output, which is equal to the difference of the applied inputs. This section discusses about the op-amp based subtractor circuit.

An op-amp based subtractor produces an output equal to the difference of the input voltages applied at its inverting and non-inverting terminals. It is also called as a **difference amplifier**, since the output is an amplified one.

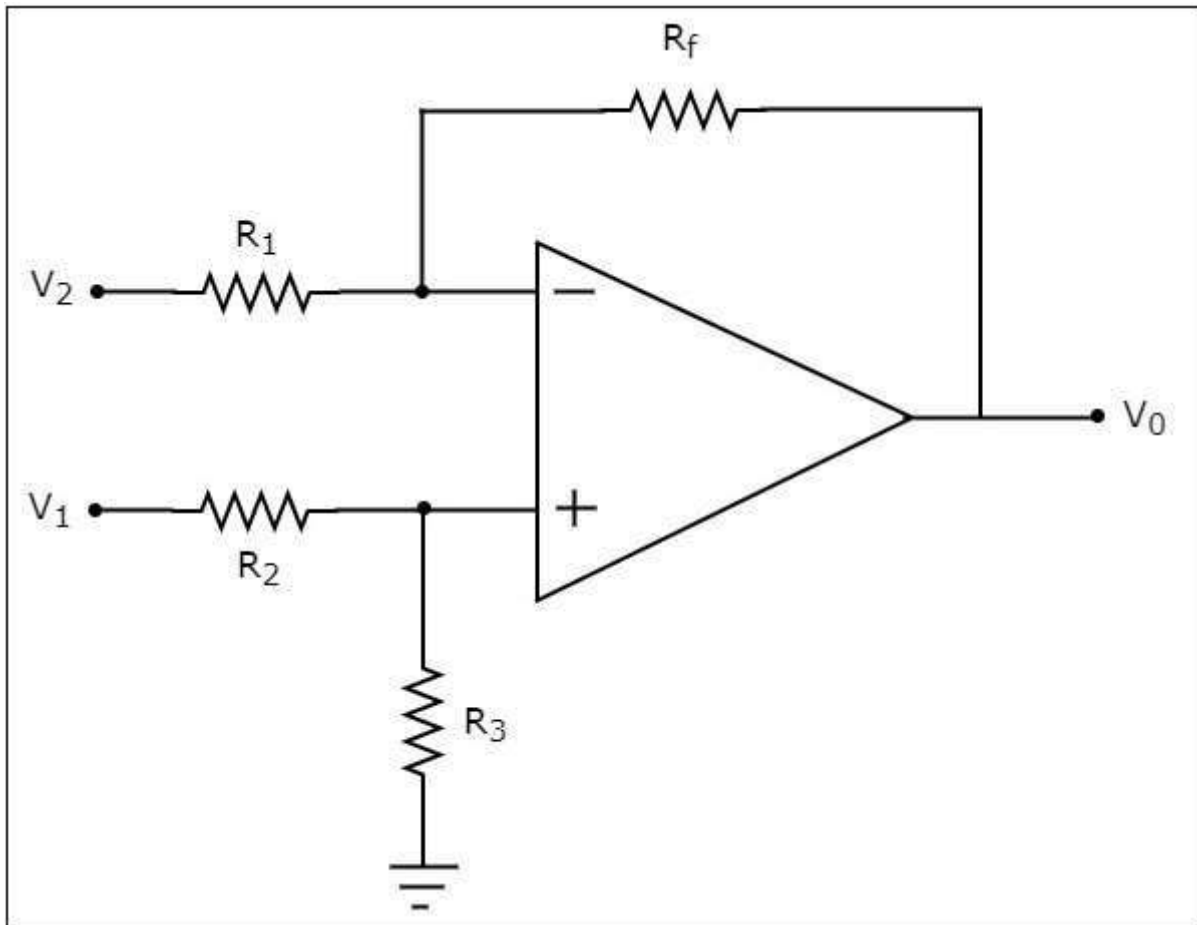The **circuit diagram** of an op-amp based subtractor is shown in the following figure –




Now, let us find the expression for output voltage  $V_0$  of the above circuit using **superposition theorem** using the following steps –
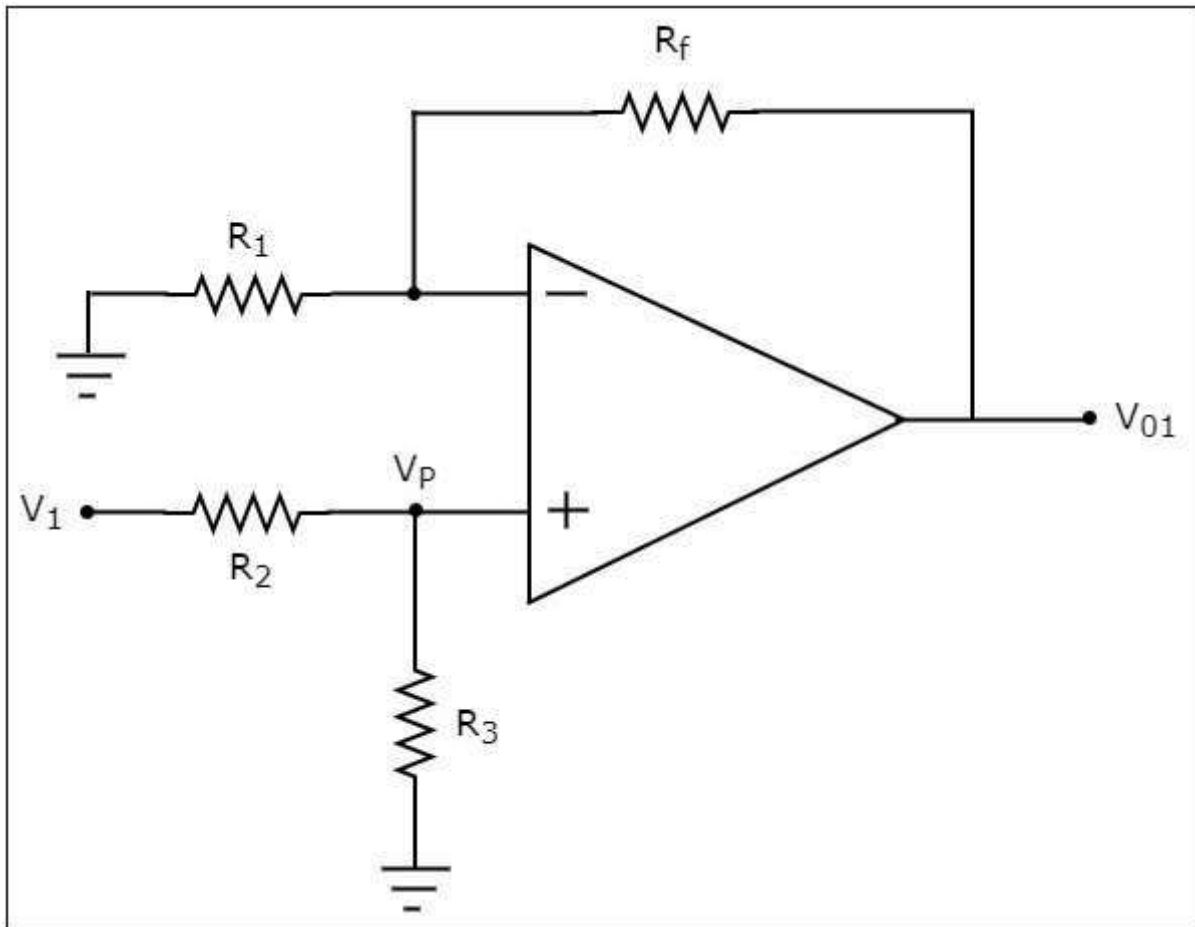
### Step 1

Firstly, let us calculate the output voltage  $V_{01}$  by considering only  $V_1$ .

For this, eliminate  $V_2$  by making it short circuit. Then we obtain the **modified circuit diagram** as shown in the following figure –



Now, using the **voltage division principle**, calculate the voltage at the non-inverting input terminal of the op-amp.

$$\Rightarrow V_p = V_1 \left( \frac{R_3}{R_2 + R_3} \right)$$

$$\Rightarrow V_p = V_1 \left( \frac{R_3}{R_2 + R_3} \right)$$

Now, the above circuit looks like a non-inverting amplifier having input voltage  $V_p$ . Therefore, the

output voltage  $V_{01}$  of above circuit will be

$$V_{01} = V_p \left( 1 + \frac{R_f}{R_1} \right)$$

$$V_{01} = V_p (1 + \frac{R_f}{R_1})$$

Substitute, the value of  $V_p$  in above equation, we obtain the output voltage  $V_{01}$  by considering


only  $V_1$ , as –

$$V_{01} = V_1 \left( \frac{R_3}{R_2 + R_3} \right) \left( 1 + \frac{R_f}{R_1} \right)$$

$$V_{01} = V_1 (R_3 R_2 + R_3) (1 + R_f R_1)$$
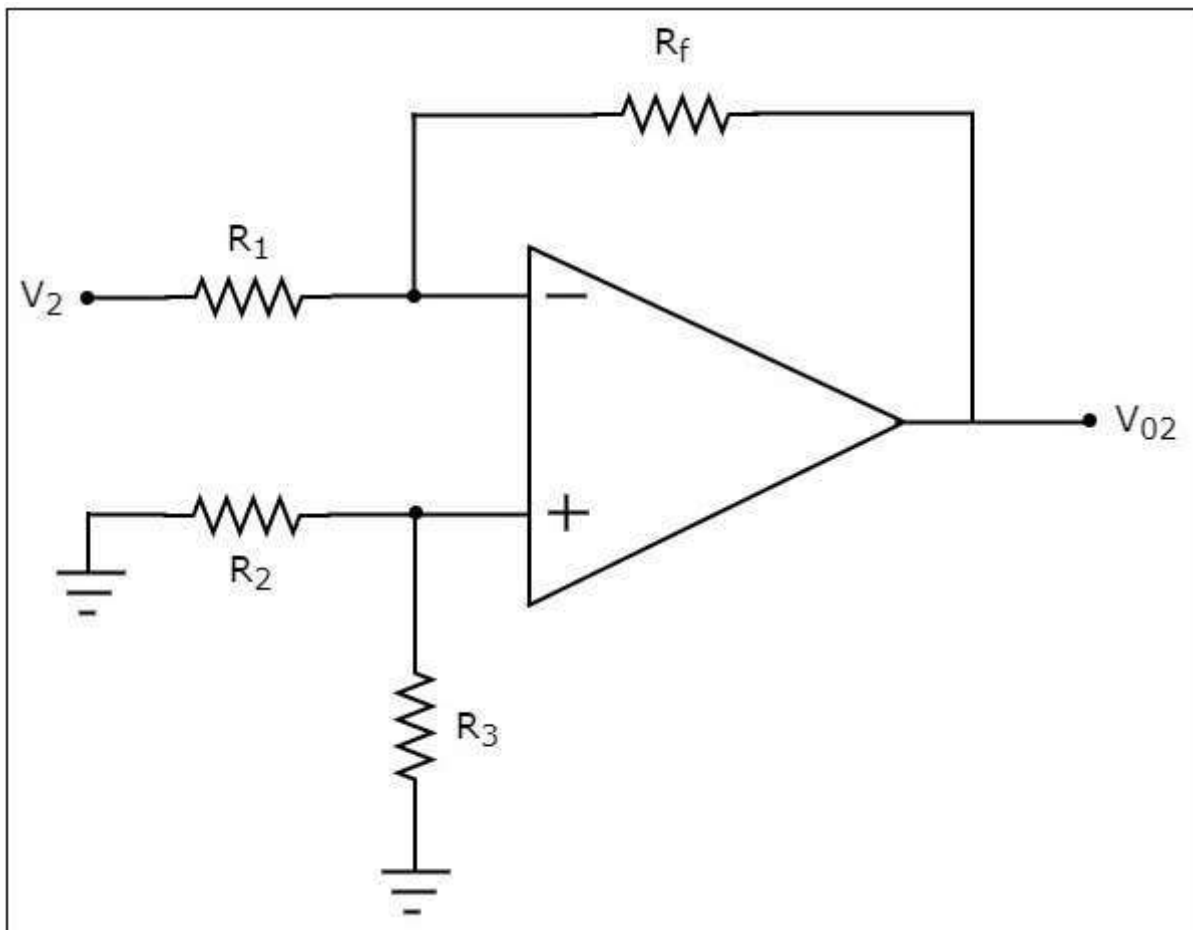
## Step 2

In this step, let us find the output voltage,  $V_{02}$   $V_{02}$  by considering only  $V_2$   $V_2$ . Similar to that in the above step, eliminate  $V_1$   $V_1$  by making it short circuit. The **modified circuit diagram** is shown in the following figure.



You can observe that the voltage at the non-inverting input terminal of the op-amp will be zero volts. It means, the above circuit is simply an **inverting op-amp**. Therefore, the output voltage  $V_{02}$   $V_{02}$  of above circuit will be –

$$V_{02} = \left( -\frac{R_f}{R_1} \right) V_2$$

$$V_{02} = (-R_f R_1) V_2$$

### Step 3

In this step, we will obtain the output voltage  $V_0$  of the subtractor circuit by **adding the output voltages** obtained in Step1 and Step2. Mathematically, it can be written as

$$V_0 = V_{01} + V_{02}$$

$$V_0 = V_{01} + V_{02}$$

Substituting the values of  $V_{01}$  and  $V_{02}$  in the above equation, we get –

$$V_0 = V_1 \left( \frac{R_3}{R_2 + R_3} \right) \left( 1 + \frac{R_f}{R_1} \right) + \left( -\frac{R_f}{R_1} \right) V_2$$

$$V_0 = V_1 \left( \frac{R_3}{R_2 + R_3} \right) \left( 1 + \frac{R_f}{R_1} \right) - \left( \frac{R_f}{R_1} \right) V_2$$

$$\Rightarrow V_0 = V_1 \left( \frac{R_3}{R_2 + R_3} \right) \left( 1 + \frac{R_f}{R_1} \right) - \left( \frac{R_f}{R_1} \right) V_2$$

$$\Rightarrow V_0 = V_1 \left( \frac{R_3}{R_2 + R_3} \right) \left( 1 + \frac{R_f}{R_1} \right) - \left( \frac{R_f}{R_1} \right) V_2$$

If  $R_f = R_1 = R_2 = R_3 = R$ , then the output voltage  $V_0$  will be

$$V_0 = V_1 \left( \frac{R}{R + R} \right) \left( 1 + \frac{R}{R} \right) - \left( \frac{R}{R} \right) V_2$$

$$V_0 = V_1 \left( \frac{R}{2R} \right) (2) - (1) V_2$$

$$\Rightarrow V_0 = V_1 \left( \frac{R}{2R} \right) (2) - (1) V_2$$

$$\Rightarrow V_0 = V_1 (2) - (1) V_2$$

$$V_0 = V_1 - V_2$$

$$V_0 = V_1 - V_2$$

Thus, the op-amp based subtractor circuit discussed above will produce an output, which is the difference of two input voltages  $V_1$  and  $V_2$ , when all the resistors present in the circuit are of same value.

## Differentiator And Integrator


The electronic circuits which perform the mathematical operations such as differentiation and integration are called as differentiator and integrator, respectively.

This chapter discusses in detail about op-amp based **differentiator** and integrator. Please note that these also come under linear applications of op-amp.
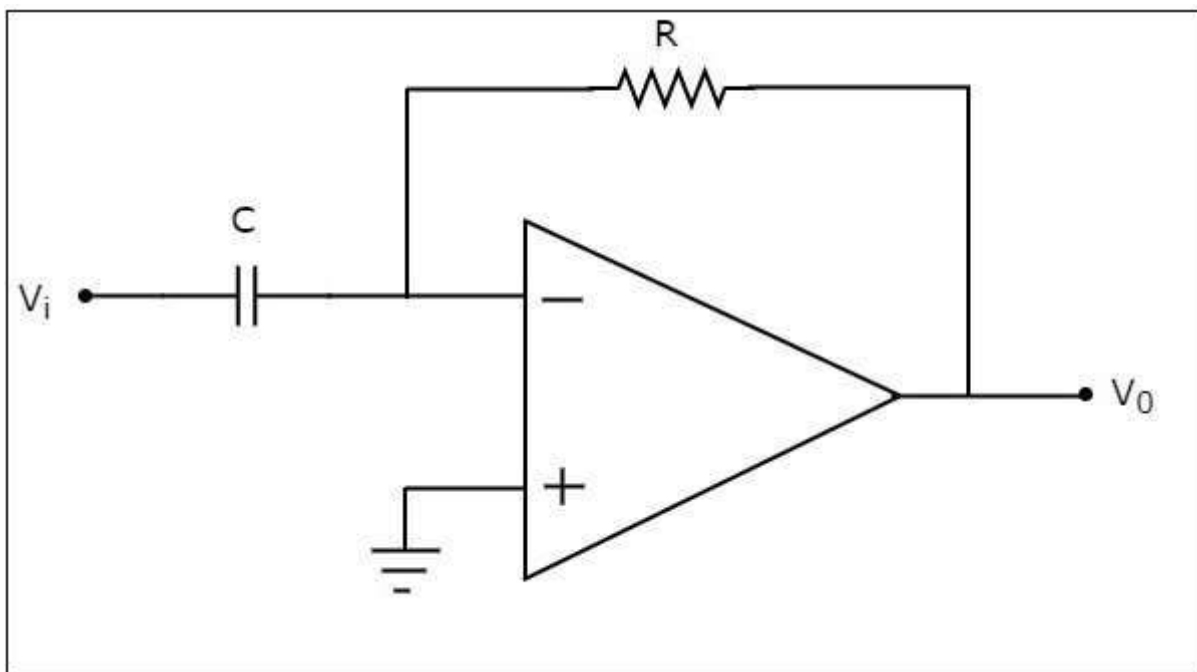
### Differentiator

A **differentiator** is an electronic circuit that produces an output equal to the first derivative of its input. This section discusses about the op-amp based differentiator in detail.

An op-amp based differentiator produces an output, which is equal to the differential of input voltage that is applied to its inverting terminal. The **circuit diagram** of an op-amp based differentiator is shown in the following figure –



In the above circuit, the non-inverting input terminal of the op-amp is connected to ground. That means zero volts is applied to its non-inverting input terminal.

According to the **virtual short concept**, the voltage at the inverting input terminal of opamp will be equal to the voltage present at its non-inverting input terminal. So, the voltage at the inverting input terminal of op-amp will be zero volts.

The nodal equation at the inverting input terminal's node is –

$$C \frac{d(0 - V_i)}{dt} + \frac{0 - V_0}{R} = 0$$

$$Cd(0 - V_i)dt + 0 - V_0R = 0$$



$$\Rightarrow -C \frac{dV_i}{dt} = \frac{V_0}{R}$$

$$\Rightarrow -CdV_i dt = V_0 R$$

$$\Rightarrow V_0 = -RC \frac{dV_i}{dt}$$

$$\Rightarrow V_0 = -RC dV_i dt$$

If  $RC = 1 \text{ sec}$   $RC=1\text{sec}$ , then the output voltage  $V_0$  will be –

$$V_0 = -\frac{dV_i}{dt}$$

$$V_0 = -dV_i dt$$


Thus, the op-amp based differentiator circuit shown above will produce an output, which is the differential of input voltage  $V_i$ , when the magnitudes of impedances of resistor and capacitor are reciprocal to each other.

Note that the output voltage  $V_0$  is having a **negative sign**, which indicates that there exists a  $180^\circ$  phase difference between the input and the output.
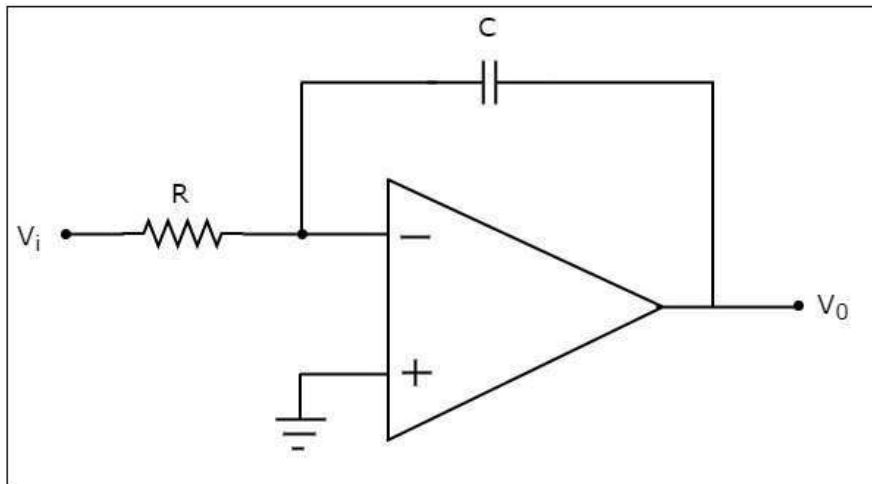
## Integrator

An **integrator** is an electronic circuit that produces an output that is the integration of the applied input. This section discusses about the op-amp based integrator.

An op-amp based integrator produces an output, which is an integral of the input voltage applied to its inverting terminal. The **circuit diagram** of an op-amp based integrator is shown in the following figure –



In the circuit shown above, the non-inverting input terminal of the op-amp is connected to ground. That means zero volts is applied to its non-inverting input terminal.

According to **virtual short concept**, the voltage at the inverting input terminal of op-amp will be equal to the voltage present at its non-inverting input terminal. So, the voltage at the inverting input terminal of op-amp will be zero volts.

The **nodal equation** at the inverting input terminal is –

$$\frac{0 - V_i}{R} + C \frac{d(0 - V_0)}{dt} = 0$$

$$0 - V_i R + C d(0 - V_0) dt = 0$$

$$\Rightarrow \frac{-V_i}{R} = C \frac{dV_0}{dt}$$

$$\Rightarrow -V_i R = C dV_0 dt$$

$$\Rightarrow \frac{dV_0}{dt} = -\frac{V_i}{RC}$$

$$\Rightarrow dV_0 dt = -V_i RC$$

$$\Rightarrow dV_0 = \left(-\frac{V_i}{RC}\right) dt$$

$$\Rightarrow dV_0 = (-V_i RC) dt$$

Integrating both sides of the equation shown above, we get –

$$\int dV_0 = \int \left(-\frac{V_i}{RC}\right) dt$$

$$\int dV_0 = \int (-V_i RC) dt$$

$$\Rightarrow V_0 = -\frac{1}{RC} \int V_i dt$$

$$\Rightarrow V_0 = -\frac{1}{RC} \int V_i dt$$

If  $RC = 1 \text{ sec}$   $RC=1\text{sec}$ , then the output voltage,  $V_0$  will be –

$$V_0 = -\int V_i dt$$

$$V_0 = -\int V_i dt$$

So, the op-amp based integrator circuit discussed above will produce an output, which is the integral of input voltage  $V_i$   $V_i$ , when the magnitude of impedances of resistor and capacitor are reciprocal to each other.

**Note** – The output voltage,  $V_0$   $V_0$  is having a **negative sign**, which indicates that there exists  $180^\circ$  phase difference between the input and the output.