

## ASSIGNMENT OF BASIC ELECTRONICS - MODULE -1 & 4

### 2<sup>nd</sup> SEMESTER, BRANCH-CSE

#### SECTION-A

**Each question carries 2 marks**

- What PN- junction diode? Draw its circuit symbols and its equivalents circuit diagram.
- Write diode current equation. Define each parameters of diode equation.
- Draw diode characteristics curve mention AC and DC resistance of diode from the graph and show Q-point.
- Write few application of LED.
- Draw the circuit diagram for finding the input and output characteristics if transistor.
- An ideal diode act as like a bi-stable switch, justify.
- Differentiate between conductor, semiconductor and insulator.
- Draw three different circuit diagrams for CC, CB, and CE configuration of BJT.
- Draw X-OR and EX-NOR gates with its truth table.
- Convert  $(1001110.011)_2 = ( )_{10}$

#### SECTION – B

**Each question carries 6 marks**

- Write short note on zener and avalanche break break-down in case of PN-junction diode.
- Write short note on Zener diode with its application.
- Draw positive and negative series clipper and explain the working principle.
- Draw common emitter transistor amplifier derive total current and show the relation between  $\alpha$  and  $\beta$ .
- Draw the input output characteristics of CE BJT amplifier draw AC, DC, load line.
- Draw half wave rectifier and explain its operation find  $I_{dc}$ ,  $V_{dc}$ ,  $I_{rms}$ ,  $V_{rms}$ ,  $P_{dc}$ ,  $P_{ac}$ , efficiency and ripple factor

#### SECTION – C

**Each question carries 16 marks**

- Draw the different types of logic gates with its truth table
- Convert the following no system  
 $(1457.238)_8 = ( )_{10}$ ?  
 $(1A05.2C4)_{16} = ( )_{10}$ ?  
 $(58.25)_{10} = ( )_8$ ?  
 $(.25.25)_{10} = ( )_2$ ?