

## Module-II (Basic Electronics)

### Field Effect Transistor

- JFET - Type (JFET → Junction Field effect Transistor)
- Operation and their characteristics

### MOSFET's

- Types
- Operation and their characteristics

### CMOS

- Brief Introduction to CMOS
- Principle of operation of digital inverters.
- VTC characteristics


### Expected Questions for Internal and Semester (Assignment)

- Q-1) Differentiate between ~~FET~~ FET and BJT ?
- Q-2) Define pinch-off voltage ?
- Q-3) Differentiate between JFET & MOSFET
- Q-4) Draw Transfer characteristic curve of n-channel and p-channel JFET.
- Q-5) Draw Drain characteristics of n-channel JFET and p-channel JFET
- Q-6) Classify MOSFET ? with its circuit and symbol.
- Q-7) Difference between Enhancement mode and Depletion Mode MOSFET with its circuit analysis and characteristics curve.

## Field Effect Transistor (FET)





- FET is a unipolar device, because its operation depends on the flow of either free electrons or, holes
- FET's are more temperature stable than BJT and are much smaller than BJT therefore suitable for use in IC
- FET's are preferred for switching application because there are no minority carriers therefore no stored charge problem.
- Less noisy
- FET input resistance is very high ( $\text{in } M\Omega$ )
- FET has smallest Gain Bandwidth product.

### Classification

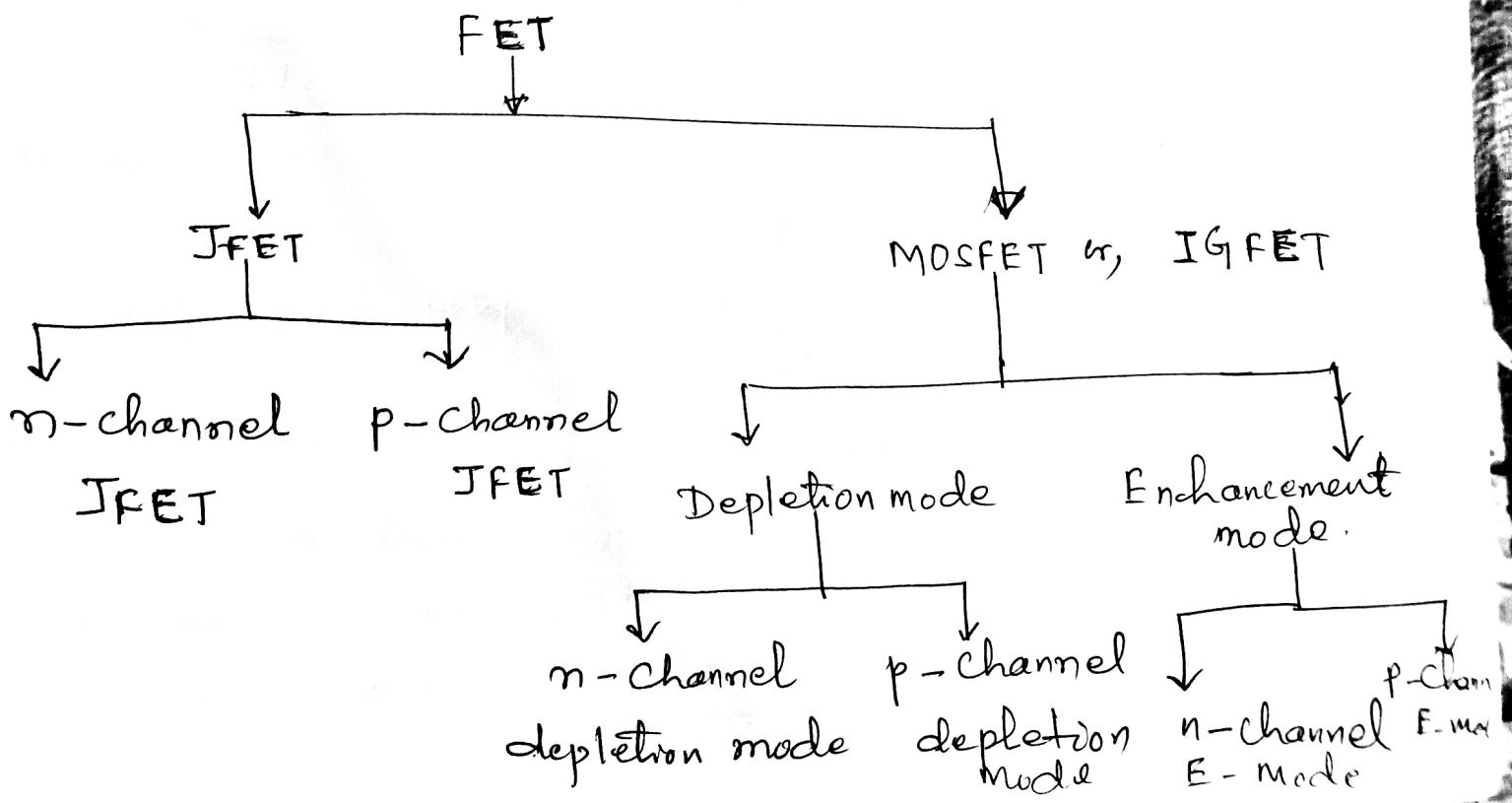


(3)


## Basic Construction :-

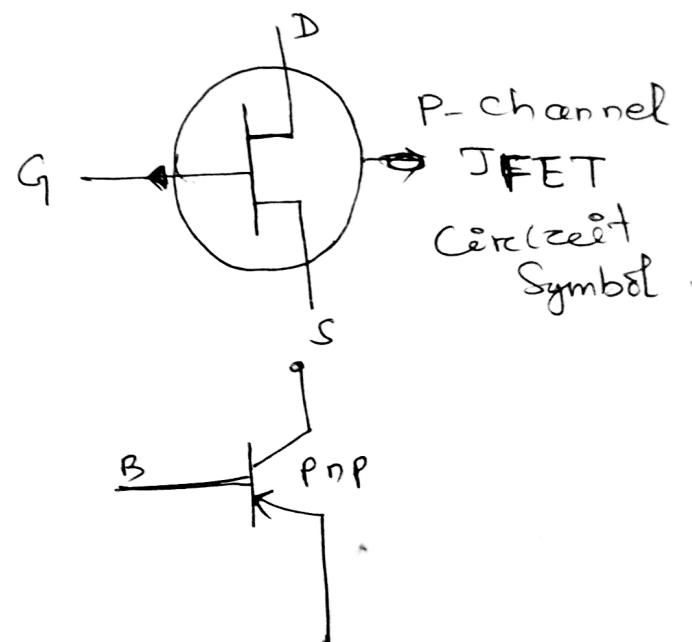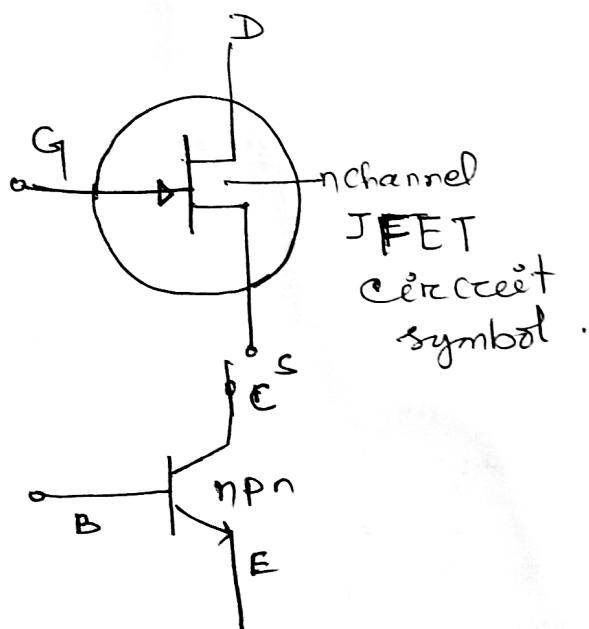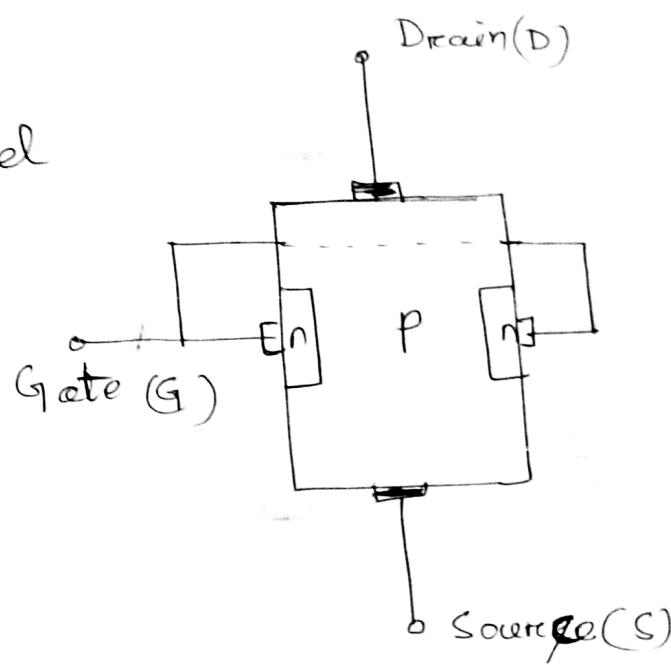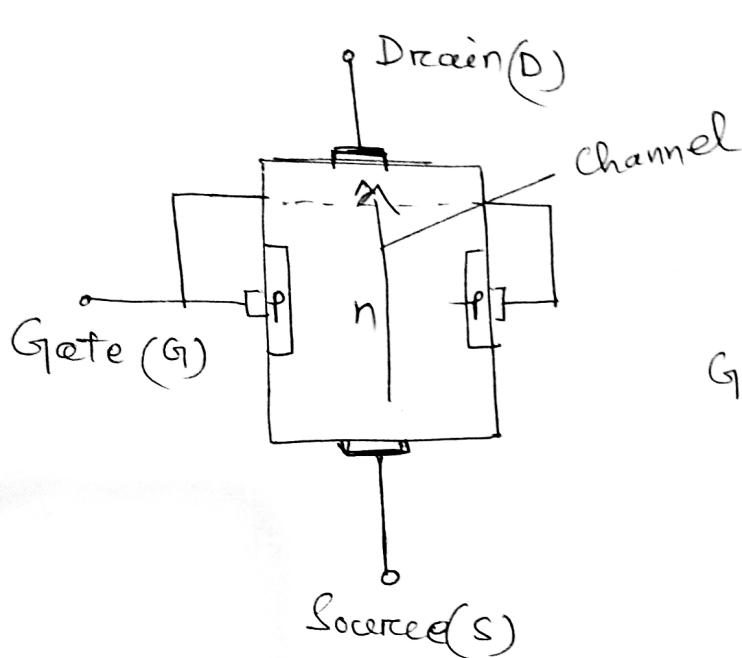

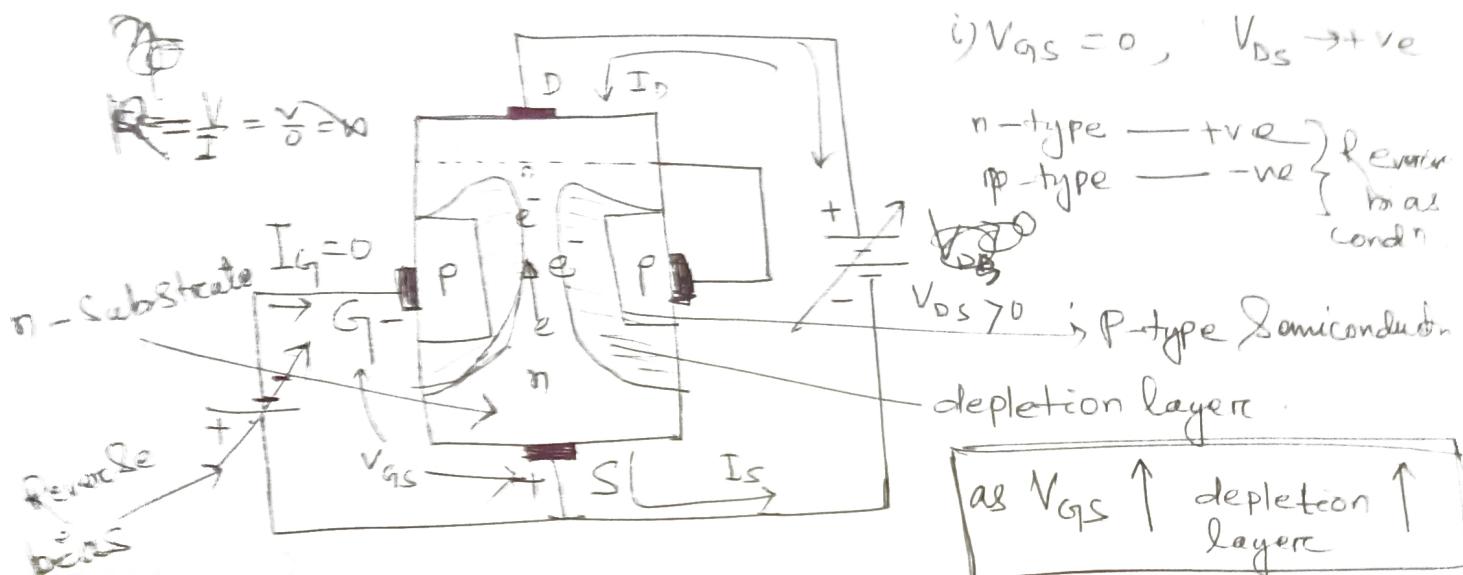
## Operation & Working Principle of n-channel JFET



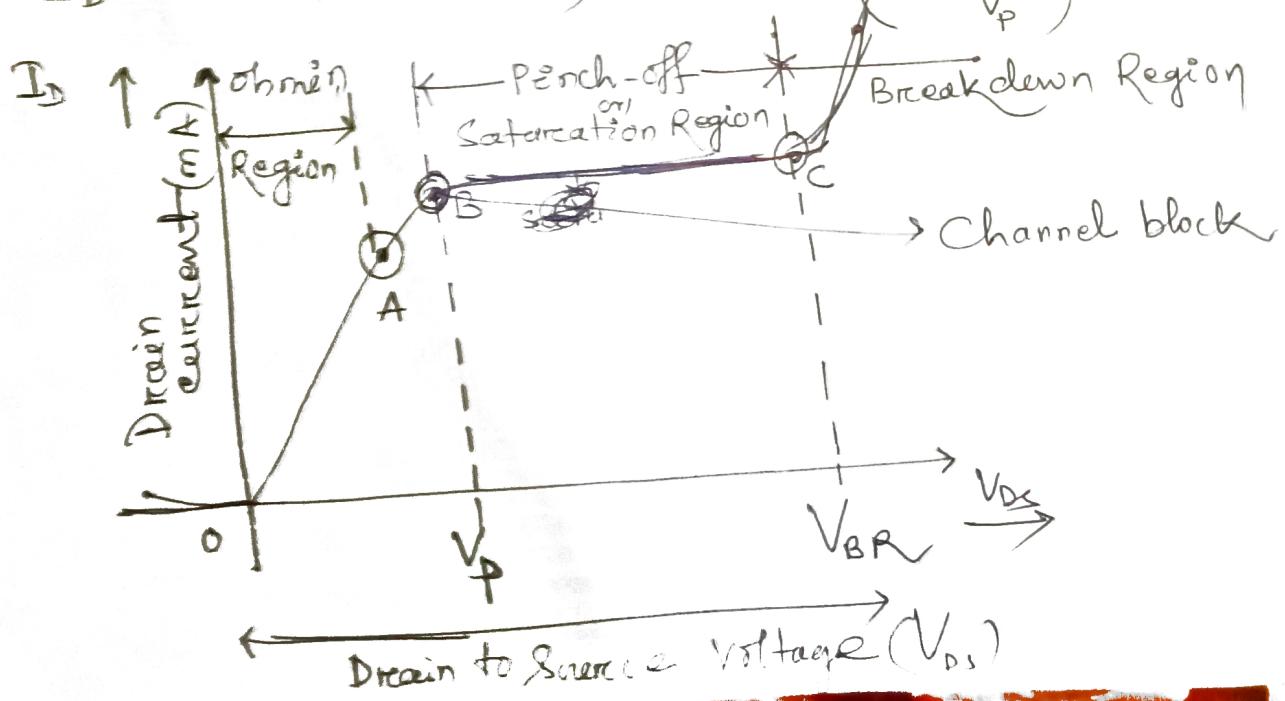- Gate-Source is reverse biased.
- The more negative the Gate voltage, the smaller current between the Source and drain
- Therefore JFET is called as a Voltage controlled device.
- When the depletion layers from both touch each other is known as pinch-off cond'n,
- $I_D$  - Drain current,  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$



(5)

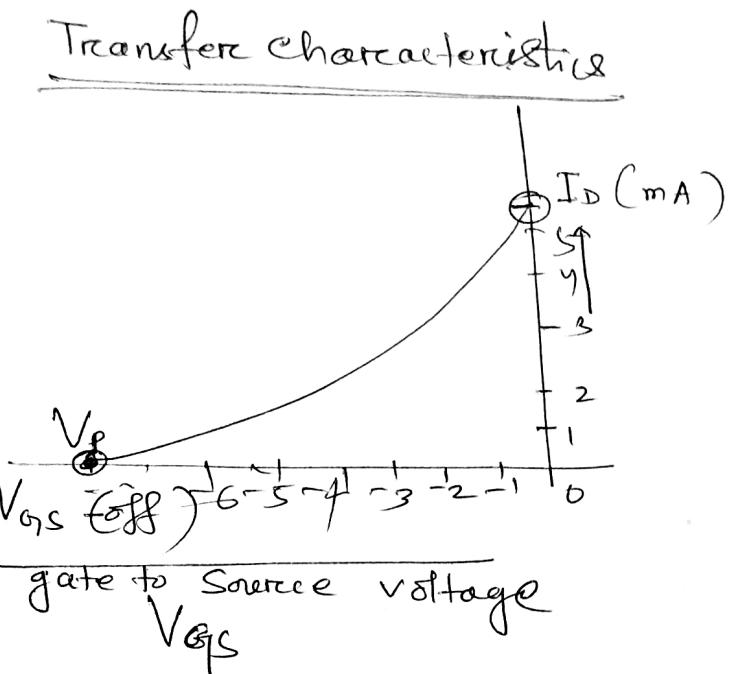


Now According Shockley equation

$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_p} \right]^2$$

- When the voltage between drain and Source terminal  $V_{DS}$ , is kept positive i.e. when  $V_{DS} > V_{GS}$  the electrons which are majority carriers in n-channel are attracted towards positive terminal of the battery  $V_{DS}$
- If further increase  $V_{DS}$ , more electrons moves towards the positive terminal of the battery  $V_{DS}$  and drain current  $I_D$  start to flow from source to drain
- $I_G = 0$  Since  $V_{GS} = 0$
- In this situation depletion region develops and the thickness of the depletion layer is more wider at the top side of n-channel and less wider at the bottom side n-channel.

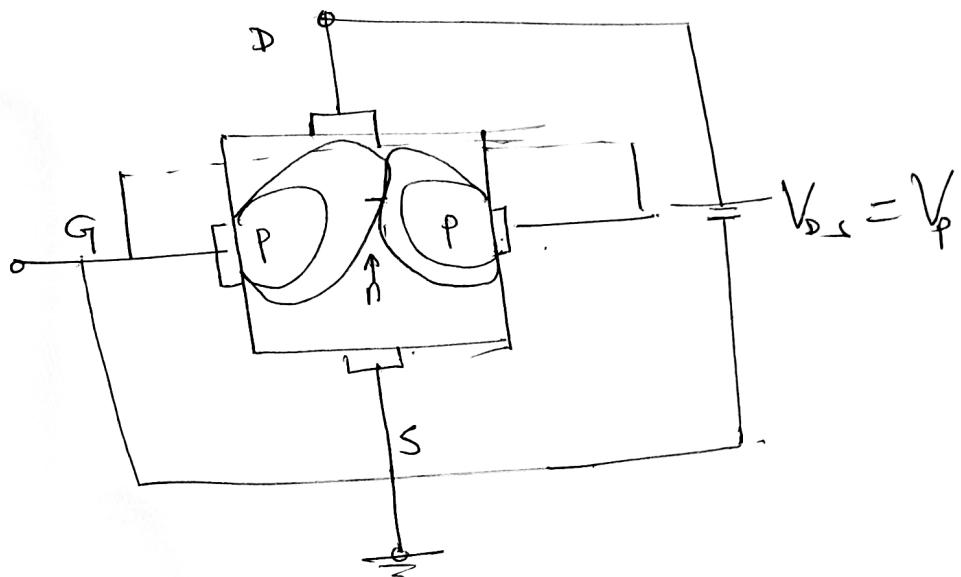(6)


→ As there is further change of drain to source voltage  $V_{DS}$ , it reaches a certain limit of voltage where depletion layer becomes much wider than they touch each other.




→ In this case n-channel is blocked and it stops flow of electrons from Source to drain through channel. As we increase  $V_{DS}$  further, the drain current  $I_D$  is not changed, it will be constant.

(2)

## P-channel JFET

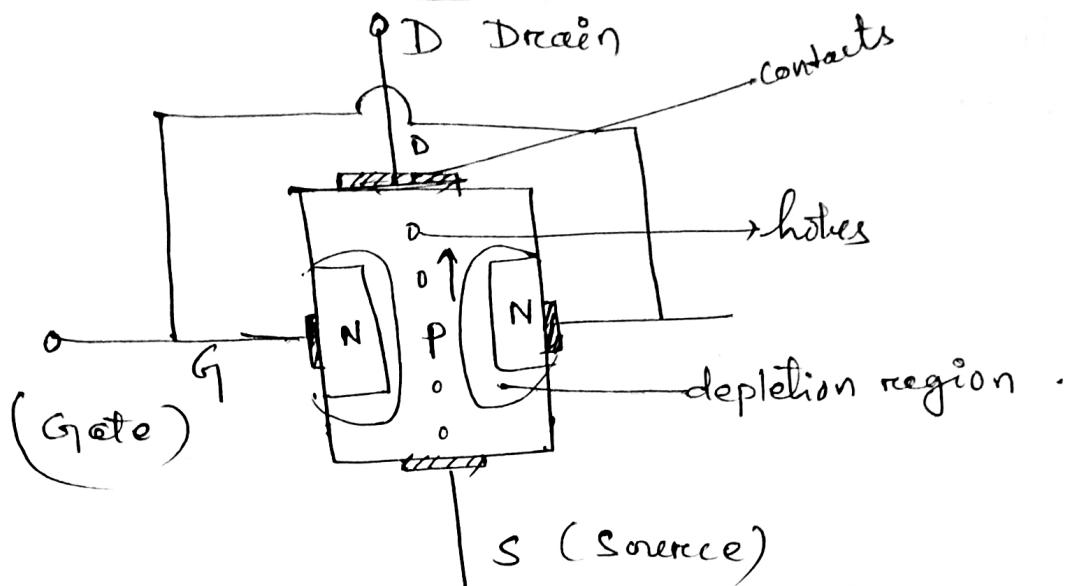

## Working of P-channel JFET

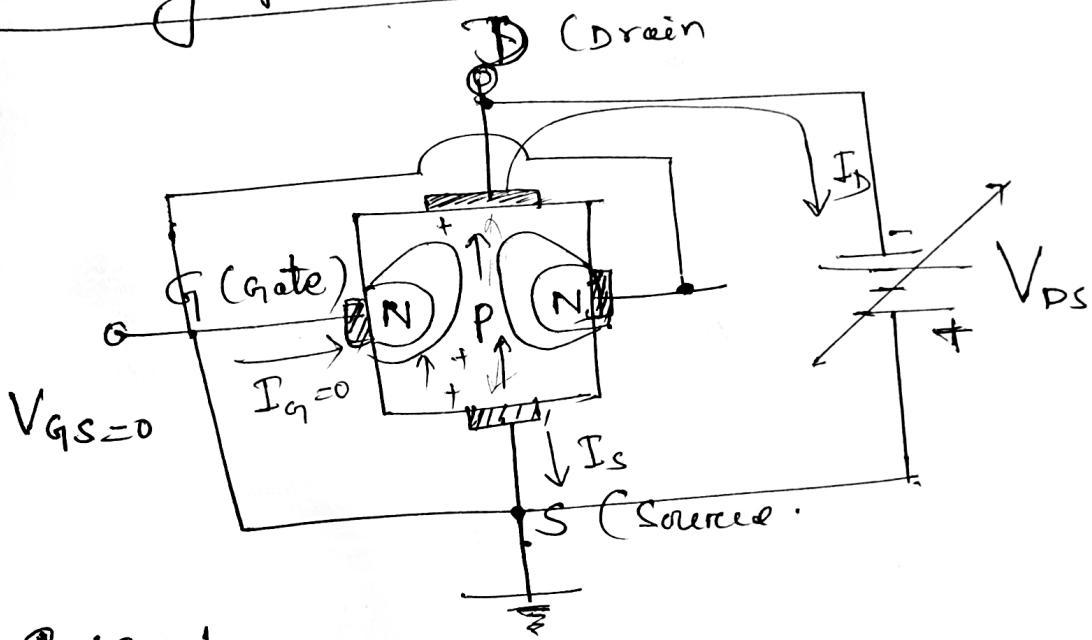Case - 1When  $V_{GS} = 0 \quad V_{DS} < 0$ 

→ In this case, the voltage between drain and Source ( $V_{DS}$ ) is kept negative, as compared to  $V_{GS}$ .

$V_{GS} = 0$ . (by short-circuiting gate and Source terminal.)

(8)

- holes are the majority carriers in p-channel are attracted towards the negative terminal of the battery  $V_{DS}$ .
- as  $V_{DS}$  increases, more holes moves towards the negative terminal of the battery and the drain current starts to flow in the same direction of holes.

~~is from Source~~.

- $I_G = 0$  since  $V_{GS} = 0$ .
- The depletion layer becomes more wider at the Top side of the p-channel and less wider at the bottom of the P-channel.
- further change in  $V_{DS}$  a certain cond<sup>n</sup> reach where the depletion layer from both side touch each other.
- In this case p-channel blocked and stops the flow of holes from source to drain through channel. (~~so~~) the drain current  $I_D$  is not changed and become constant.

~~Case-2 (When  $V_{GS} > 0, V_{DS} < 0$ )~~



- when  ~~$V_{GS} >$~~ .  $V_{GS}$  becomes more positive, and  $V_{DS}$  is more negative, depletion layer at both side touch each other. The constant current start to flow before  $V_P$ .

Case-2


(9)

$$V_{GS} > 0$$

$$V_{DS} < 0$$

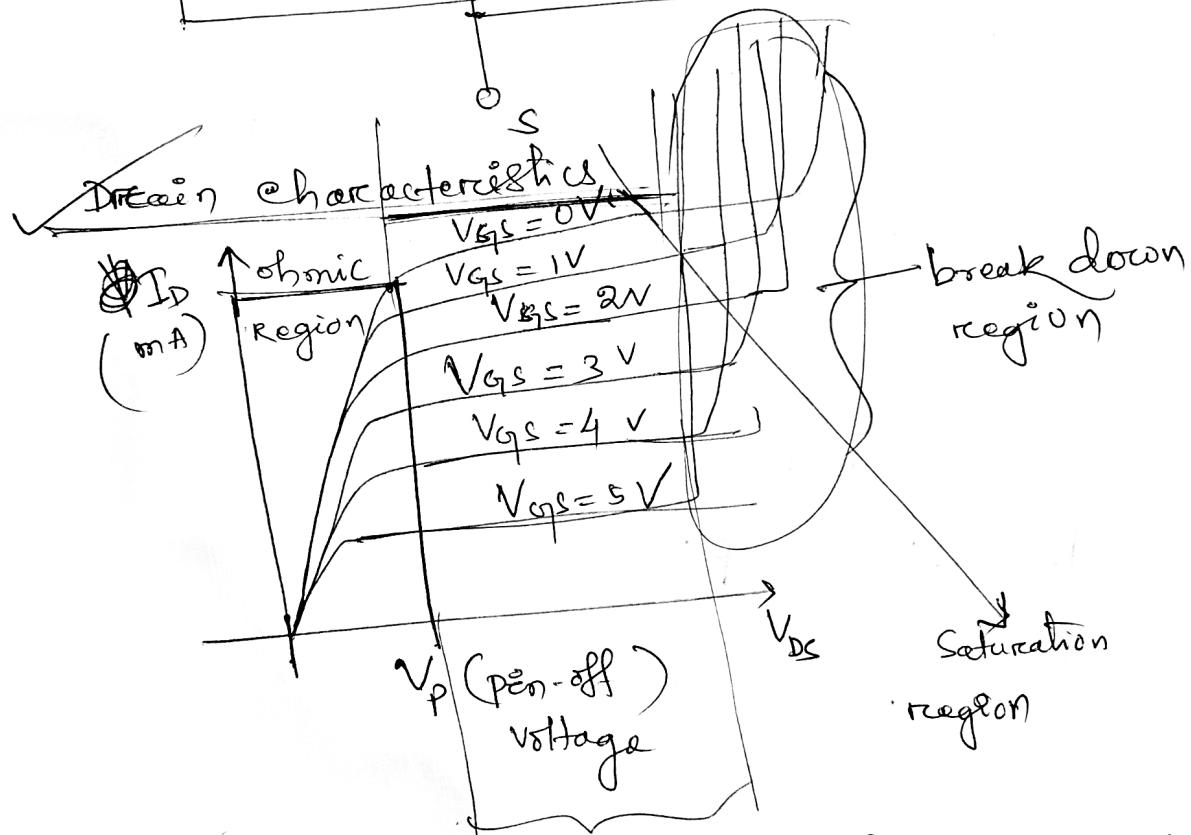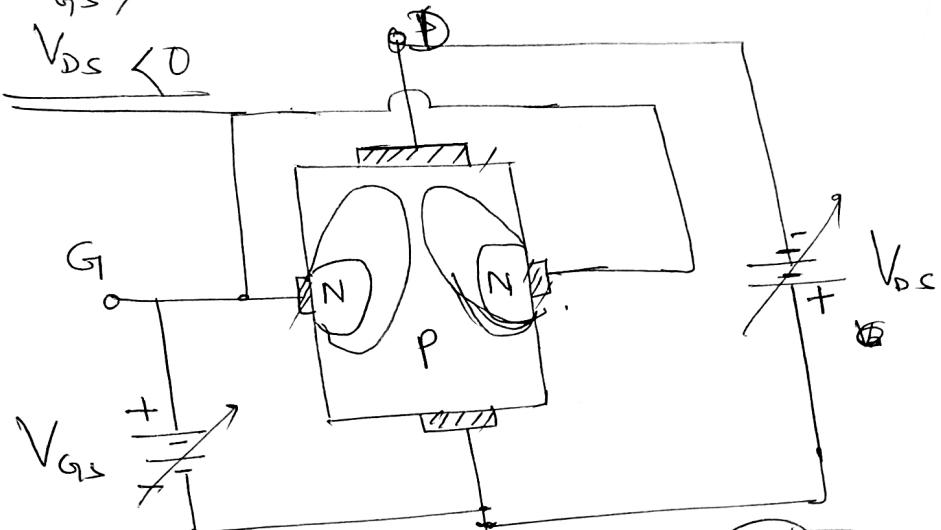

Transfer characteristic

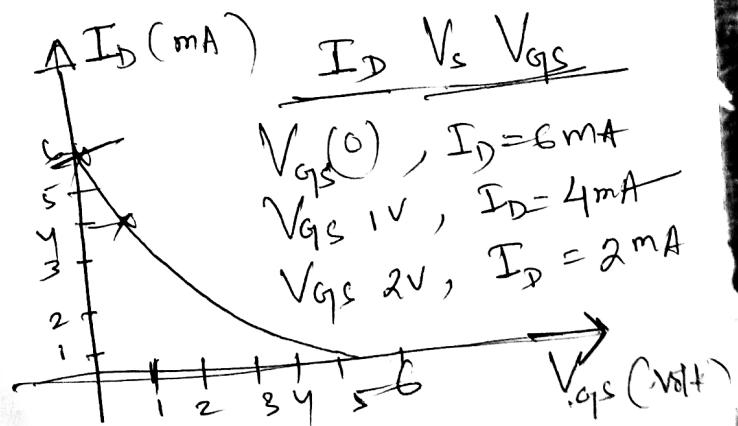


(10)

## MOSFET:-

- MOSFET → stands for Metal oxide Silicon field effect transistor.
- It is also called IGFET - insulated Gate field effect transistor.
- It operates both in enhancement mode and depletion mode of operation.


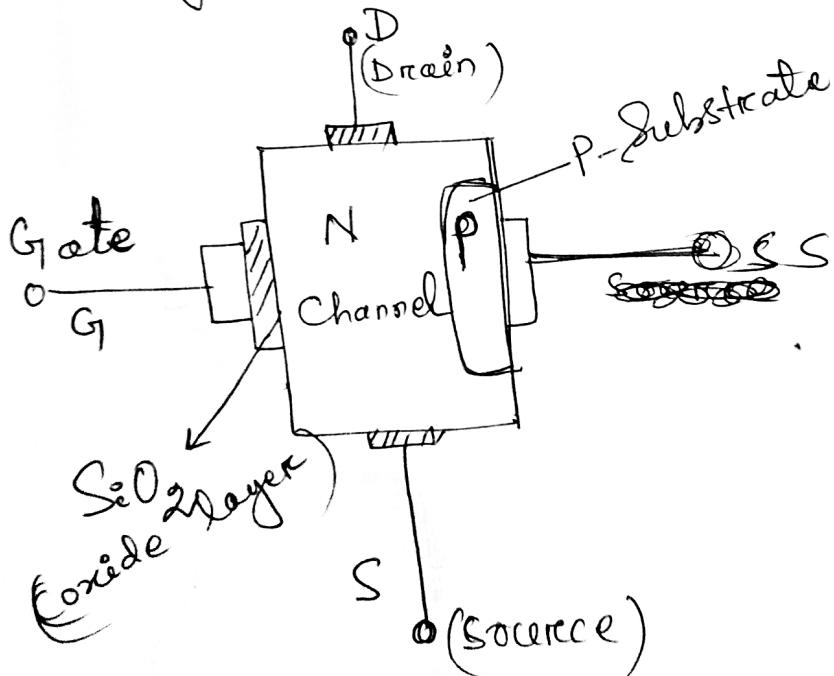
### Construction :-

- The construction is very similar to JFET
- An oxide layer is deposited on the substrate which gate is connected.




- The voltage at gate controls the operation of MOSFET.
- both positive and negative voltages can be applied on the gate.

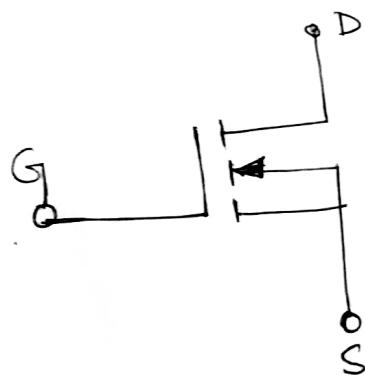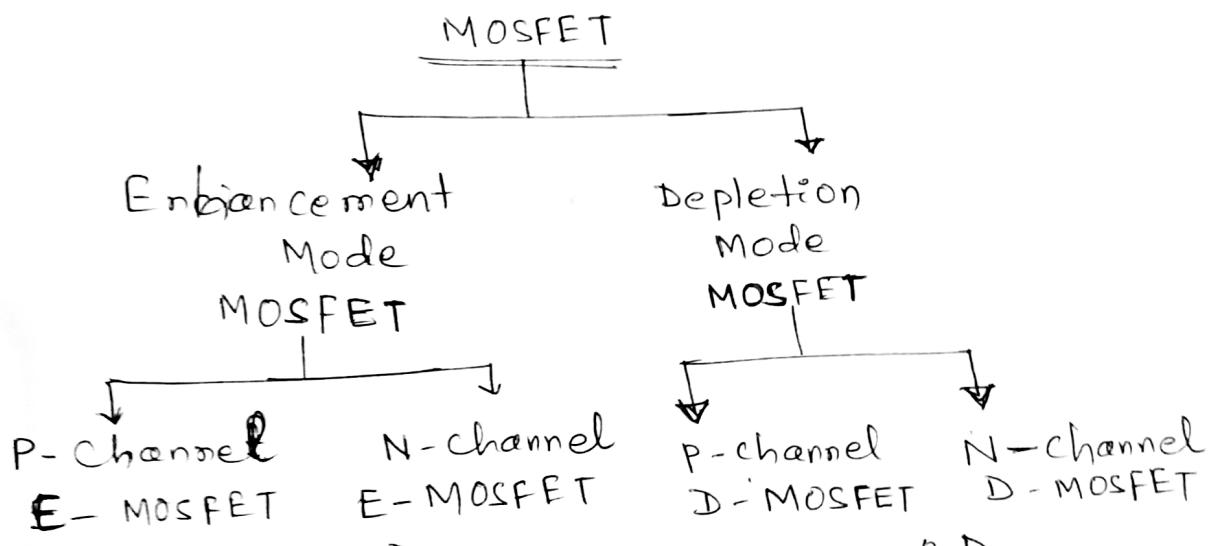- With negative gate bias voltage it act as depletion MOSFET
- With positive gate bias voltage it act as Enhancement MOSFET
- Classification




Enhancement  
Mode (MOSFET)

N-channel MOSFET

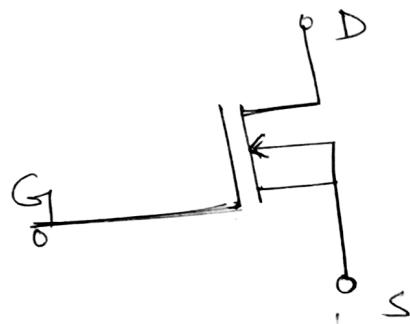

Depletion Mode

(MOSFET)

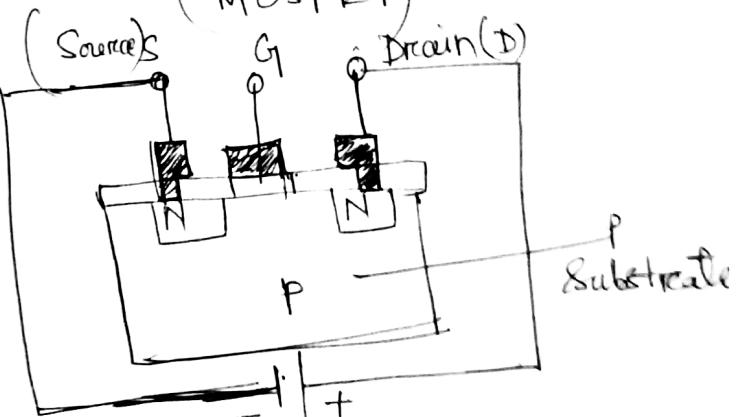


18


(12)

Write Short Note on


### Enhancement type MOSFET

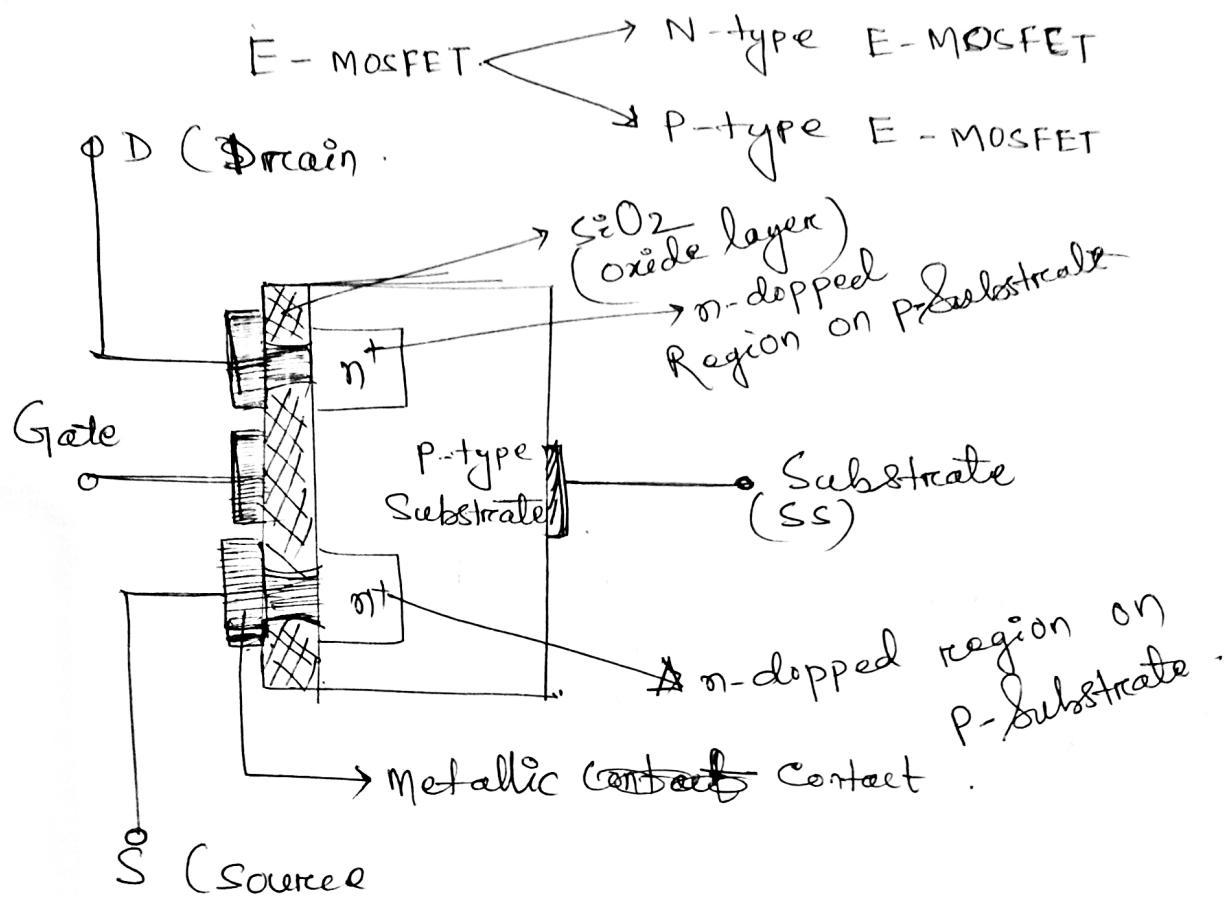

Symbol

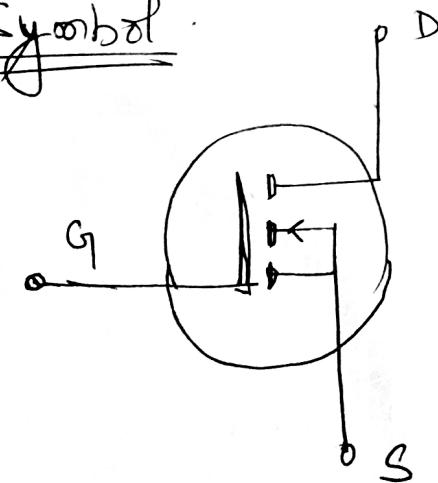


n-channel E - MOSFET

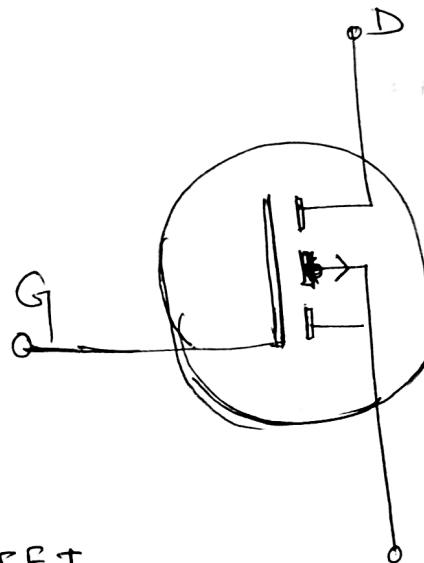

P - channel  
S E - MOSFET

(13)

## Operation of E-MOSFET

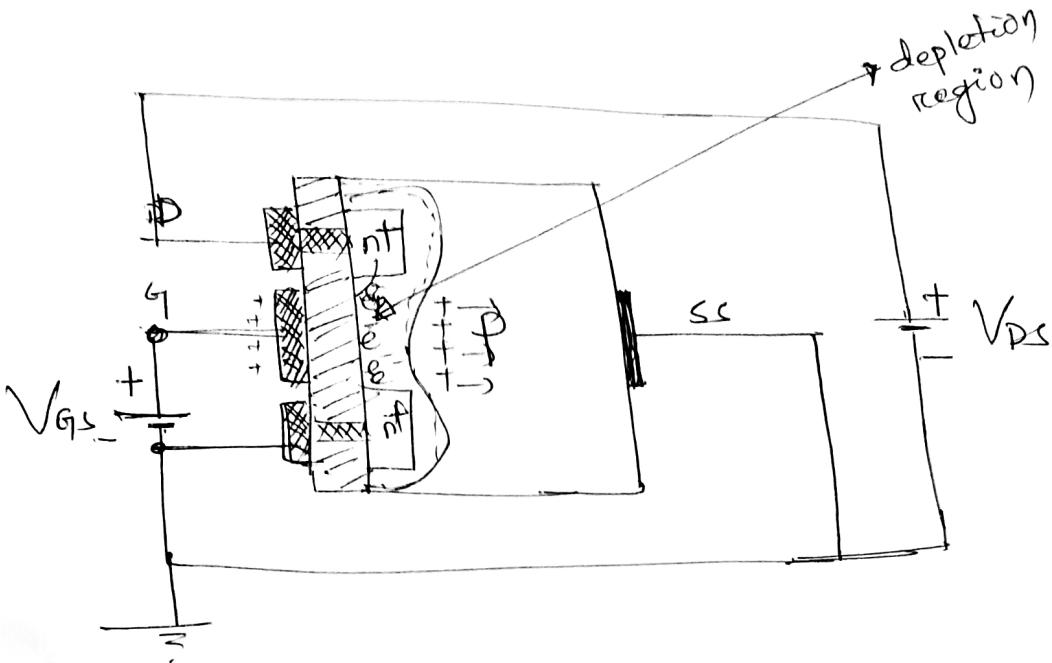

→ If  $V_{GS} = 0V$ , and  $V_{DS} = +Ve$ , no current flows.

due to absence of channel. (all the electrons gets attracted to the gate terminal)

→ If  $V_{GS} = +ve$ ,  $V_{DS} = +ve$   
all the electrons from N-well and p-substrate well get attracted towards the Gate terminals.

→ The level of  $V_{GS}$  at which the channel begins to conduct e.g. called threshold voltage  $V_T$

When  $V_{DS} > V_T$ , the electron well starts to flow the channel.

→ Since the channel non-existent with  $V_{GS} = 0$  and it is enhanced by the application of a +ve gate to Source voltage, this type of MOSFET is called as Enhancement type MOSFET

(W)

→ As  $V_{GS}$  is increased beyond the threshold level, the density of free carriers in the induced channel will increase resulting in an increased level of drain current.


→ If we hold  $V_{GS} = \text{constant}$

and Increase the ~~level~~ level of  $V_{DS}$   
following condition occurs

→ If  $V_{DS} < V_{GS} - V_T$

i.e linear region

$I_D \uparrow$  with  $V_{DS} \uparrow$



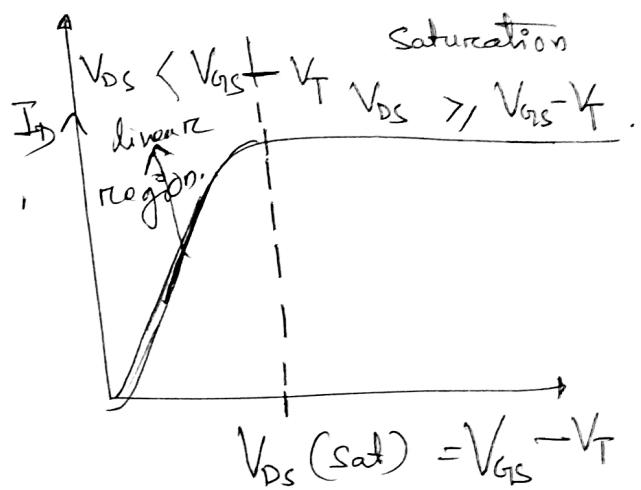


→  $V_{DS} = V_{GS} - V_T$ , when the channel pinched off


→  $V_{DS} > V_{GS} - V_T$ , Saturation region

$I_D = \text{constant}$ ,  $V_{DS} \uparrow$

Drain Characteristics

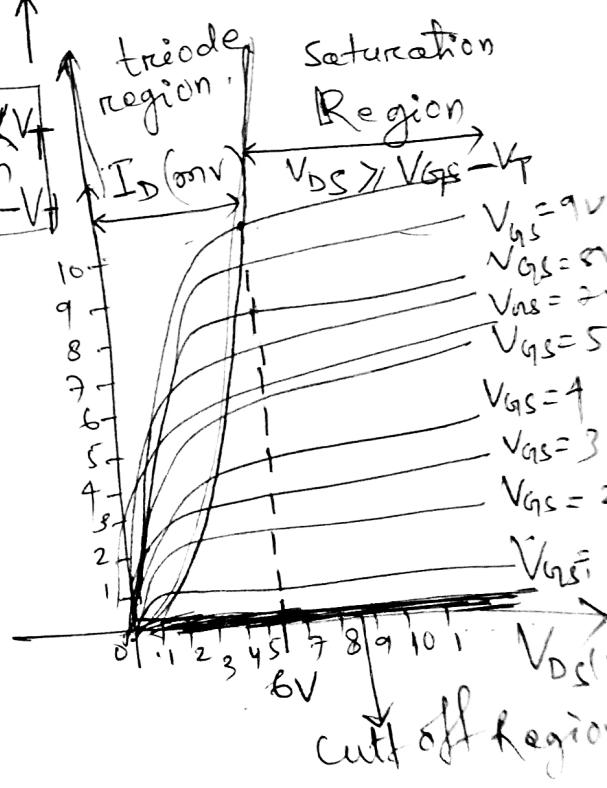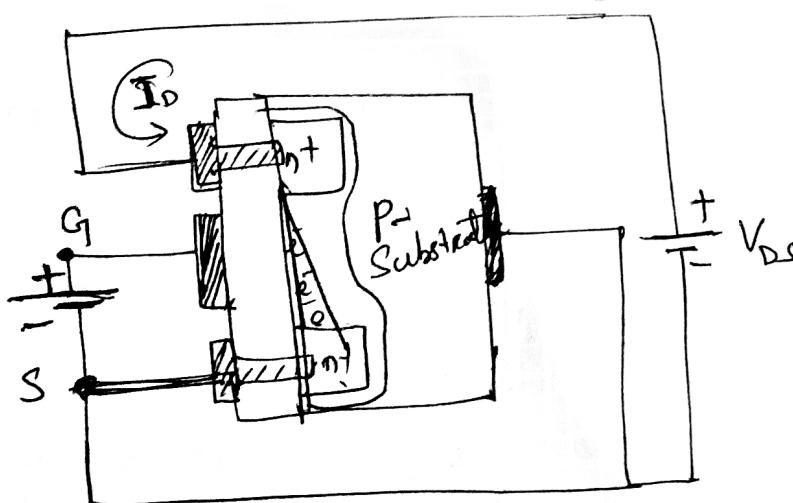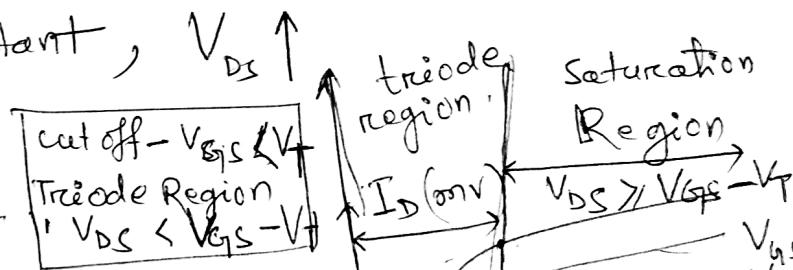

## Transfer characteristics of E-MOSFET

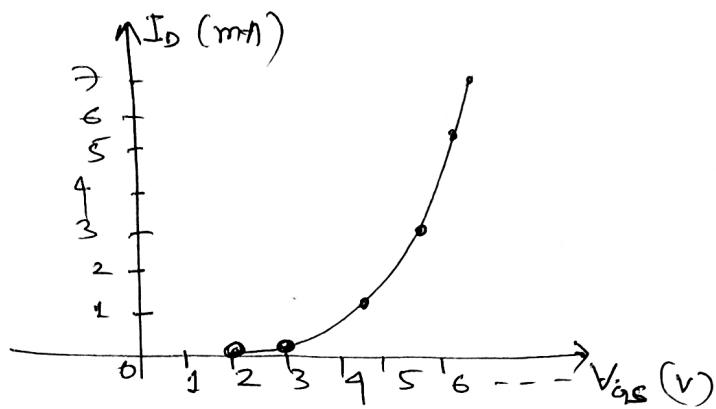


The Drain current is related to applied gate-to-source voltage by the following non-linear relationship

$$I_D = k(V_{GS} - V_T)^2$$


Where  $k$  = constant

## P-channel Enhancement type MOSFET

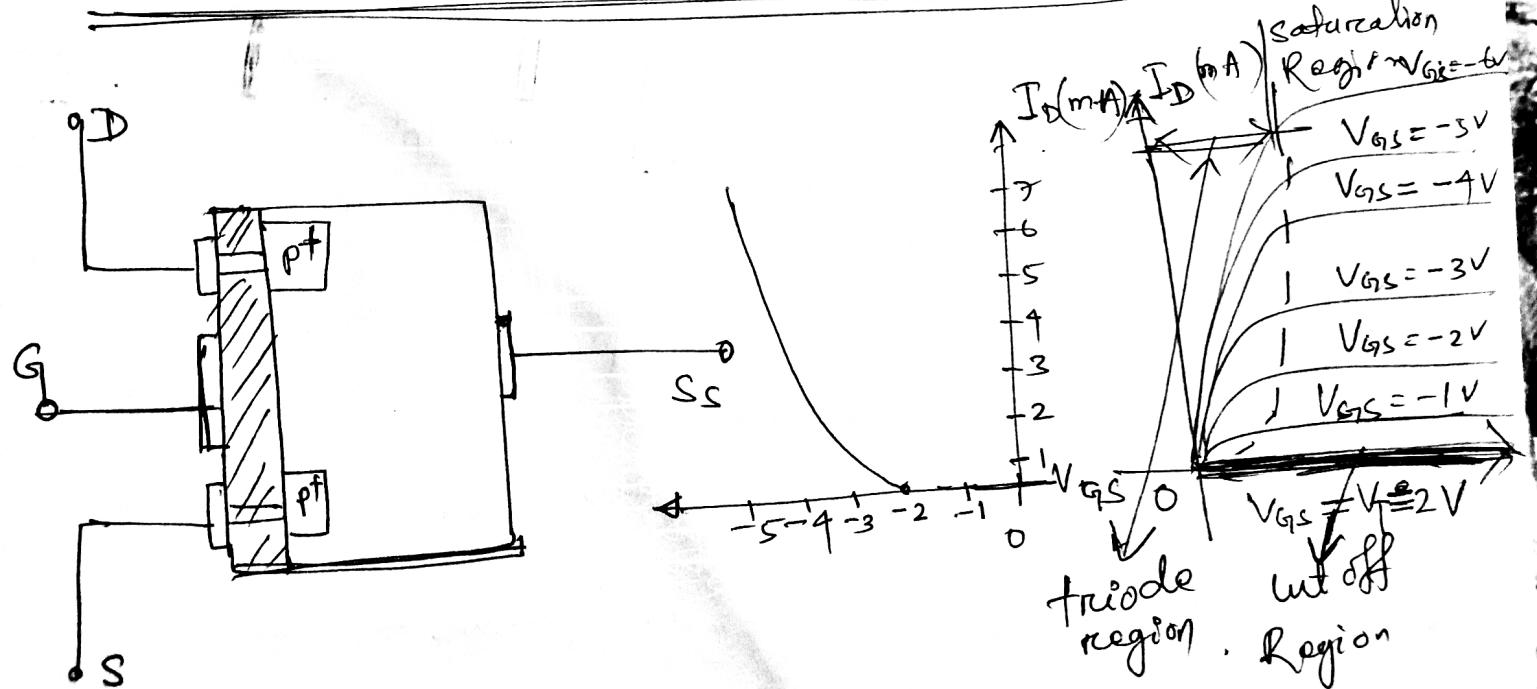

# Depletion type MOSFET :-

## construction

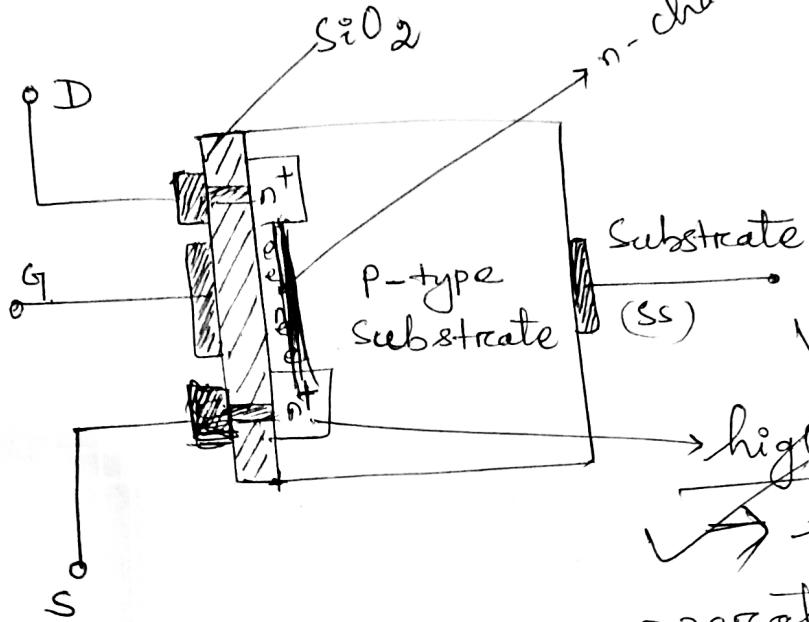

When the gate terminal is given positive potential at  $V_{GS}$ , then the drain source voltage  $V_{DS}$ , then due to the repulsion,


In depletion occurs due to which flow of current reduce

highly doped n-region


hence works in depletion Mode.

## operation

### Symbol

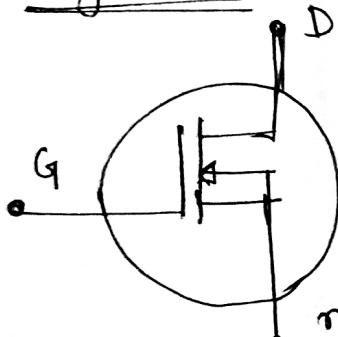

n-channel  
depletion type  
MOSFET

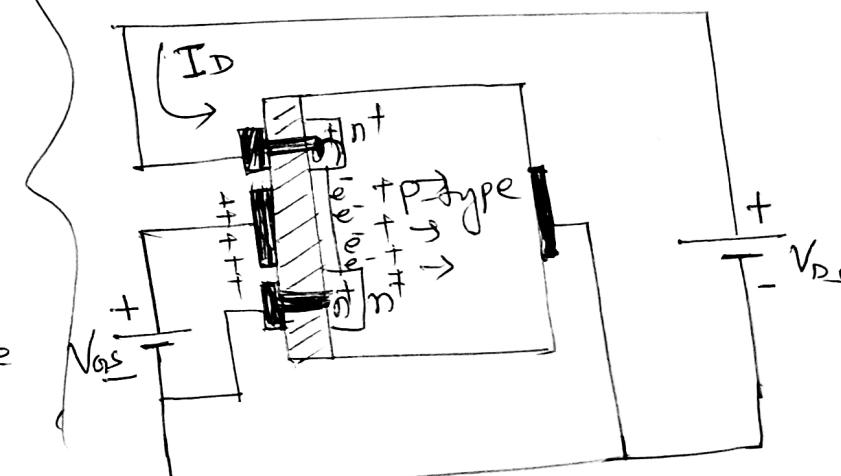


→ Operation with  $V_{GS} = 0$

$$V_{DS} = +ve$$


→ Operation with  $V_{GS} = +ve$ ,  $V_{DS} = +ve$

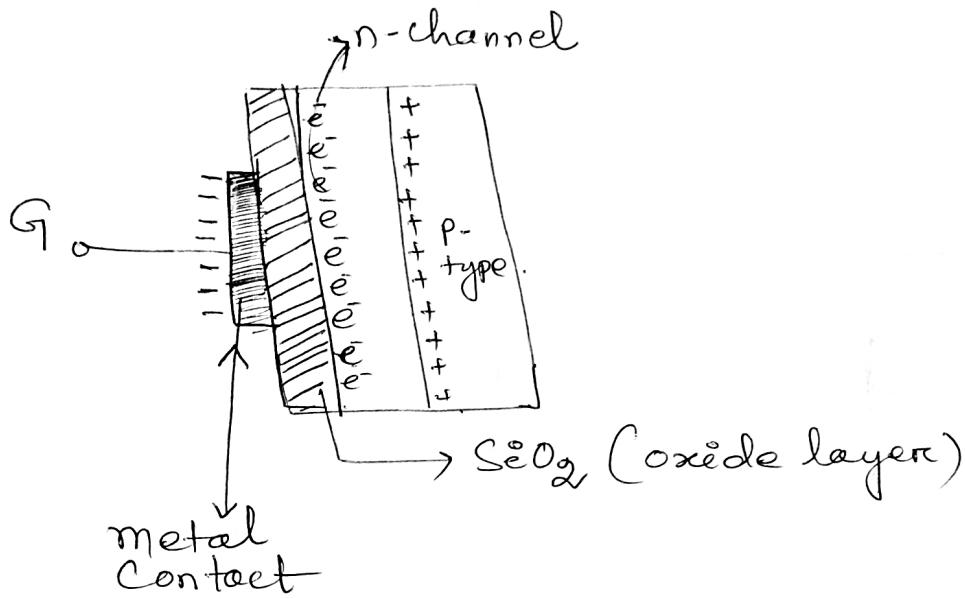→ Operation with  $V_{GS} = -ve$ ,  $V_{DS} = +ve$






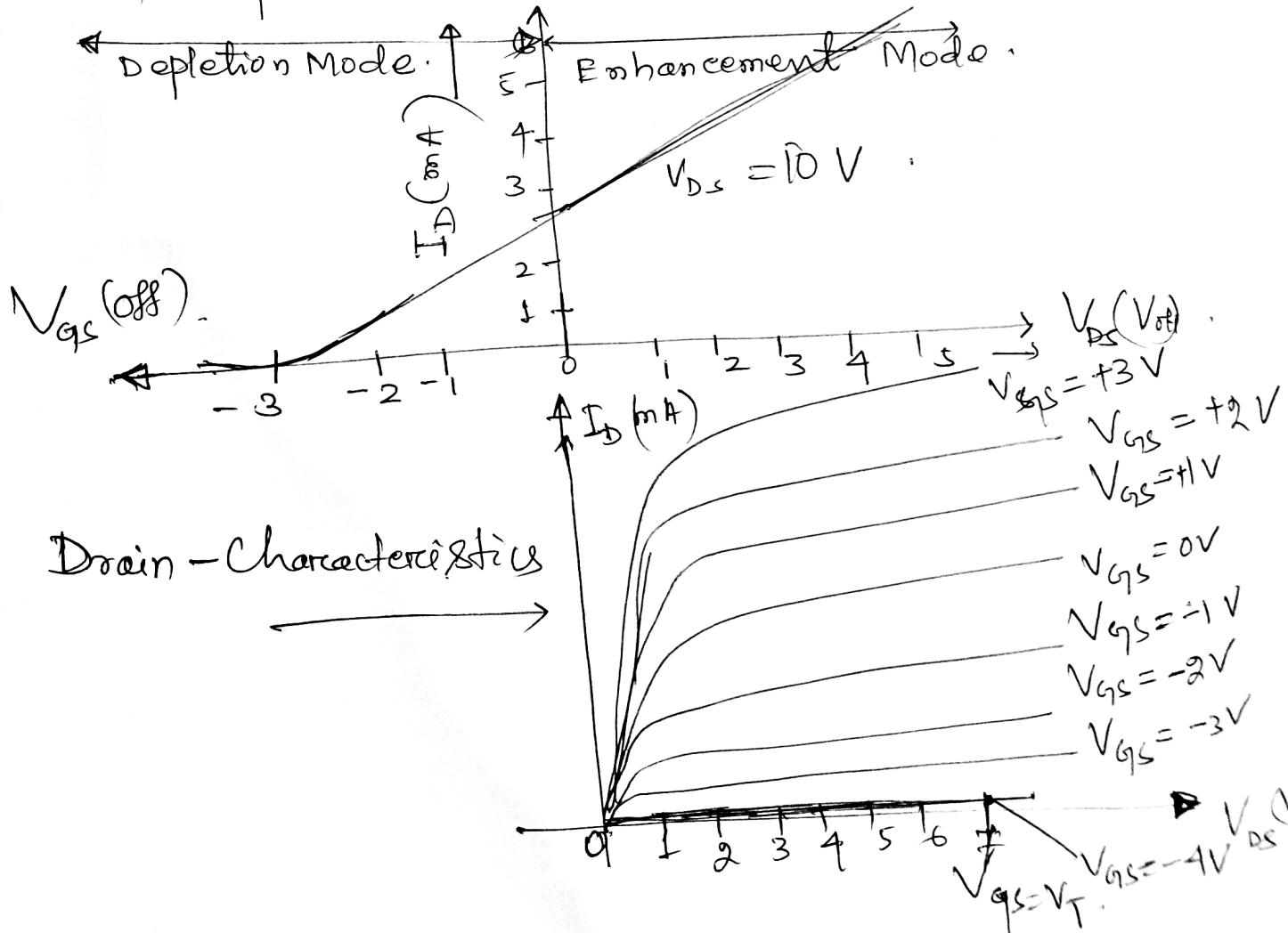
### Transfer characteristics —

Transfer characteristics define the change in the value of  $V_{DS}$  with the change in  $I_D$  and  $V_{GS}$  in both depletion and enhancement mode.



## P-channel depletion Type MOSFET

(18)

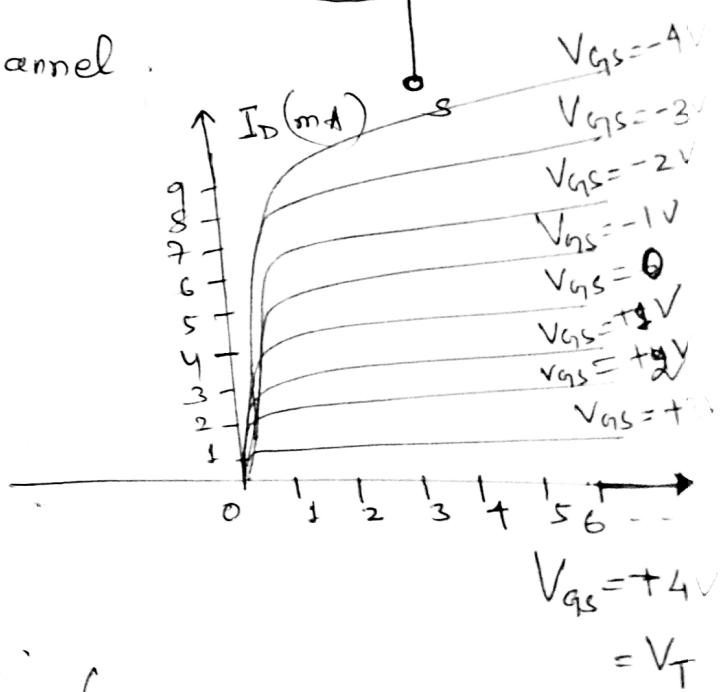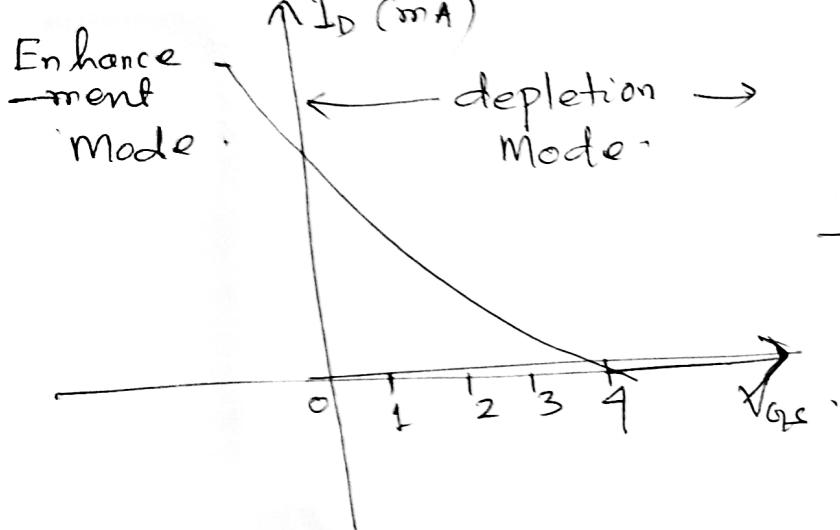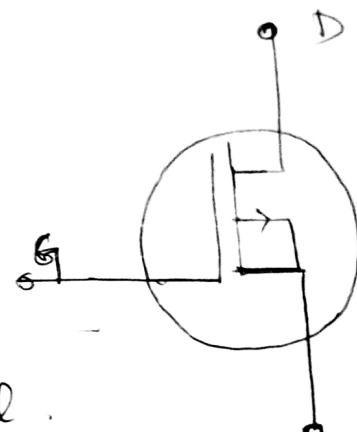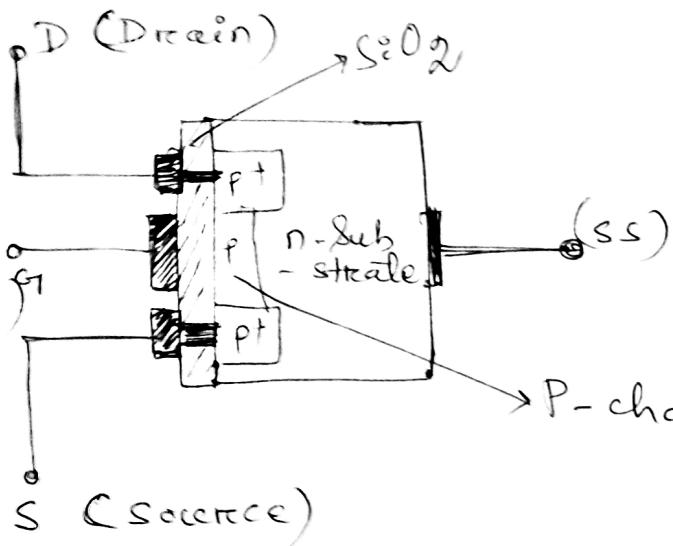

Drain - characteristic curve

& Short Note on  
⑧ inverter using CMOS