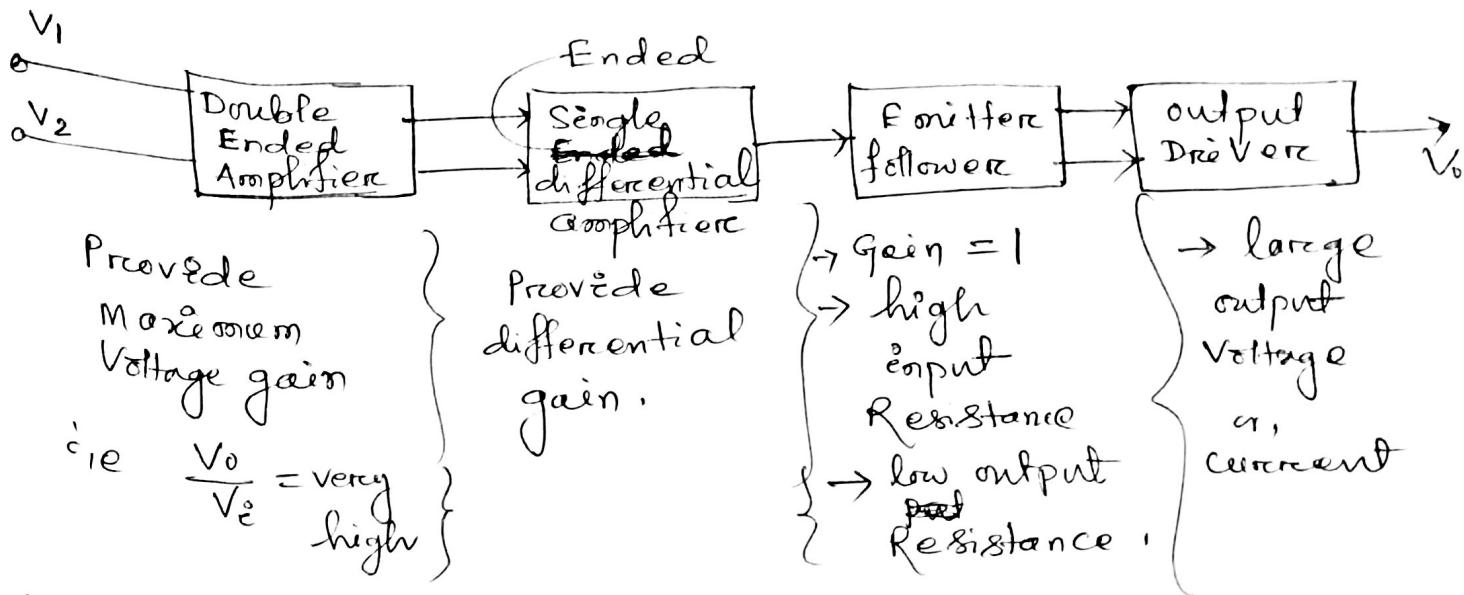


MODULE - III (BE)

1

BASIC BLOCK-diagram of OP-AMP (Operational amplifier)




6 marks

Parameters of OP-Amp

The parameters of OP-Amps are

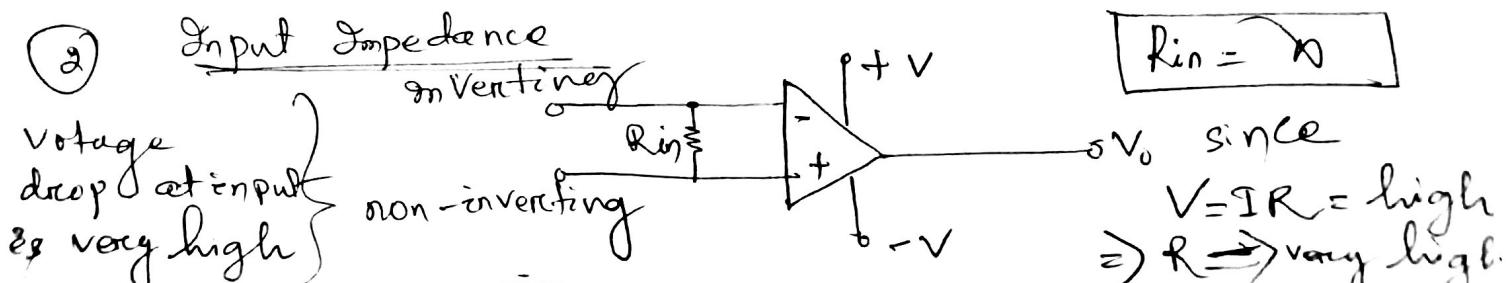
- 1) ~~Voltage gain~~
- 2) Input resistance (impedance)
- 3) output impedance,
- 4) Input offset voltages
- 5) Input offset current
- 6) Input Bias current
- 7) Bandwidth.

① Voltage gain \Rightarrow Gain =
$$\frac{\text{Output Voltage}}{\text{Input Voltage}}$$



③ Output Impedance

(2)

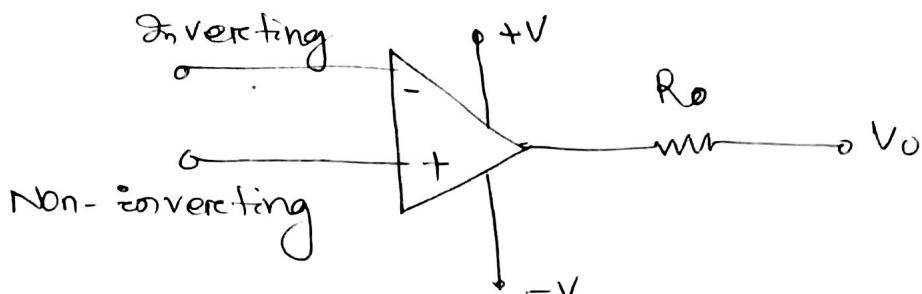

$$R_o = \text{output impedance}$$

- The resistance offered by the output of an op-amp is called as ~~as~~ output impedance.
- All the output of an op-amp must be passed to the next device.
- The voltage drop at output must be 0


i.e., $V_{out} = 0$

$$\Rightarrow V \times R = 0$$

$$\Rightarrow \cancel{R}$$

→ R should be very very low

④ Input Offset Voltage

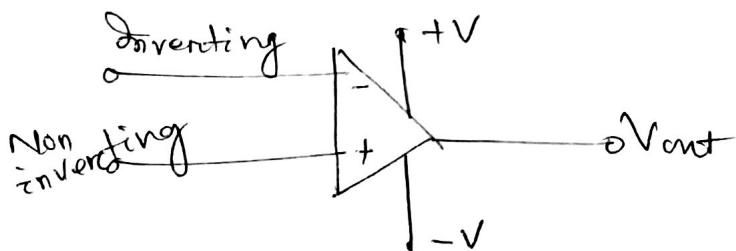


} if i/p Voltage \neq 0 Volt
 \Rightarrow out voltage should be zero voltage (ideal)
 (practical Non zero)

- ⇒ we need to apply some dc voltage at the input terminal to ~~force~~ force the output voltage to be Zero. This applied voltage is called as input-offset voltage.

(3)


(5) Input offset current

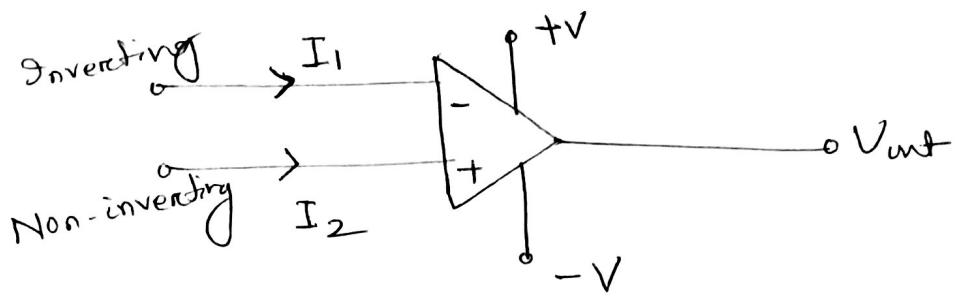

$$\text{Input offset Current} = \boxed{I_1 - I_2} \quad \text{OR} \\ \boxed{I_2 - I_1}$$

The difference between the currents onto the two terminals when output is held at zero is called as "input offset current".

(6) Input Bias Current

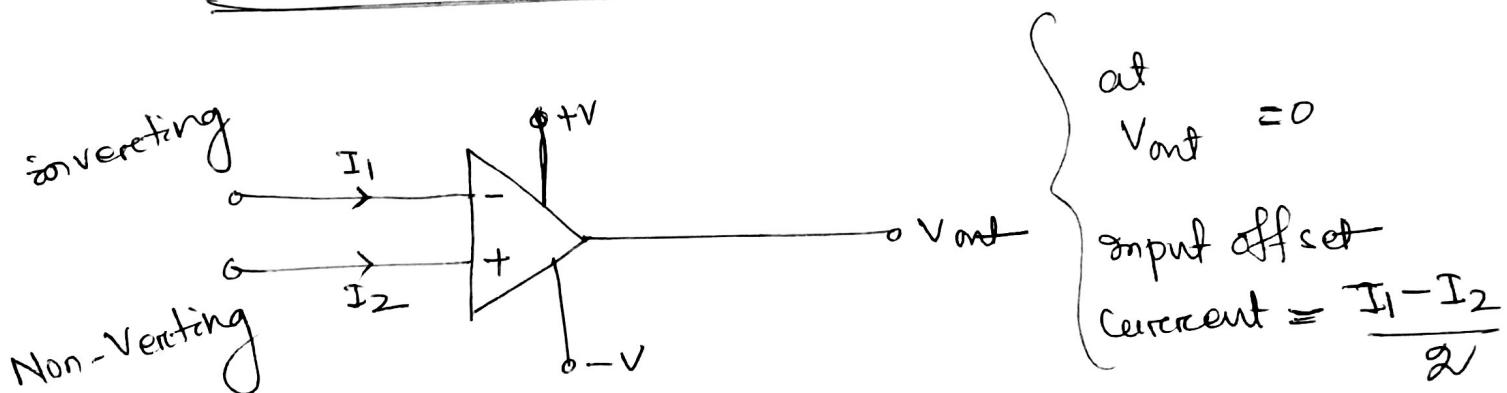

The average of the current onto the two input terminals with the output at zero volt is called as input Bias current.

7) Bandwidth

The range of frequencies for which an op-amp can be used is called as Bandwidth of an op-amp.

| Parameters | Ideal OP-Amp | Practical OP-Amp |
|------------------------|--------------|--------------------------|
| → Voltage gain | → ∞ | → very high |
| → Input impedance | → ∞ | → $2M\Omega$ (very high) |
| → Bandwidth | → ∞ | → 1 MHz |
| → Output impedance | → zero | → 75Ω |
| → Input offset voltage | → zero volt | → 2 mV |
| → Input offset current | → zero Amp | → $20 nA_{op}$ |
| → Input bias current | → zero | → $80 nAmp$ |

Q8 Write few properties of An Ideal OPAMP.

(Ans)

- (i) - infinite (∞) i/p impedance
- (ii) Zero output impedance.
- (iii) infinite open-loop gain.
- (iv) infinite Bandwidth.
- (v) Zero noise contribution
- (vi) Zero DC output offset voltage and current
- (vii) \rightarrow CMRR (Common-mode Rejection Ratio)


2/6

15

What is OP-Amp? write few applications of
OP-Amp

(Ans) OP-Amp stands for Operational Amplifier.

Symbol

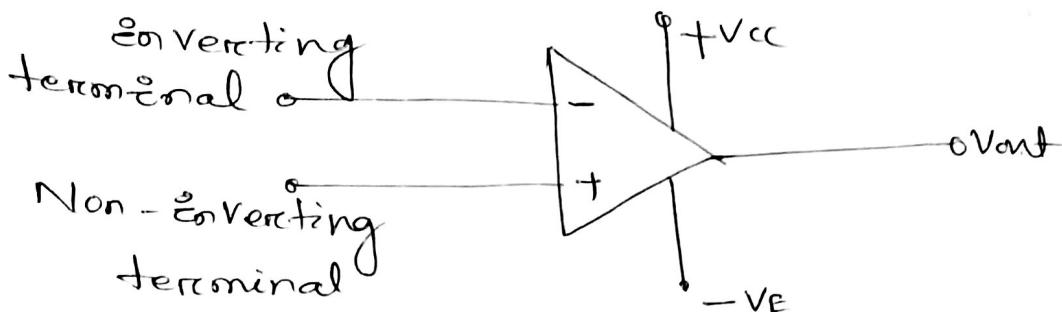

→ It is an electronic device that can perform various mathematical operations such as

- addition
- subtraction
- integration
- differentiation


→ OP-Amp can also be used for a variety of applications such as

- AC and DC signal amplification
- an active filter
- oscillators
- Regulators
- Comparators
- Converters ~~.....~~

~~Q~~ 2 marks


Q - Define CMRR (Common Mode Rejection Ratio)

$$CMRR = \frac{A_{oL}}{A_{CM}}$$

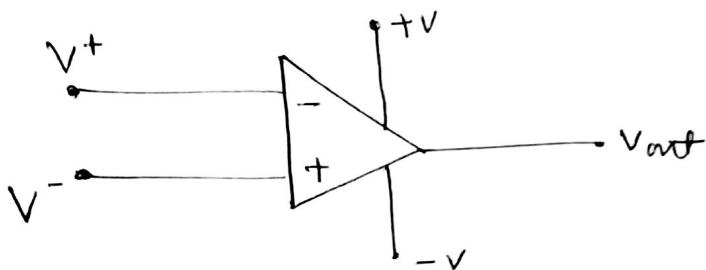

Open loop gain

$$A_{oL} = \frac{V_{out}}{V^+ - V^-}$$

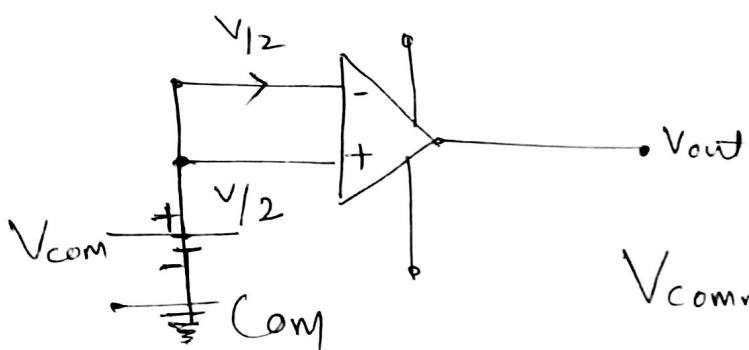

V_{common}

$A_{CM} = \text{common mode gain}$

$$A_{CM} = \frac{V_{out}}{V_{com}}$$

$$V_{common} = \frac{V_{+} - V_{-}}{2}$$

$A_{oL} = \text{open loop voltage gain}$


$A_{CM} = \text{common mode voltage gain}$.

Generally, the op-Amp has two input terminals

which ~~are~~ are positive and negative terminal and the two ~~is~~ inputs are applied at the same point. This give the opposite polarity signals at the output. Hence the ~~the~~ positive and negative voltages of the terminals will cancel out and it will give the resultant output

(7)

OPAMP P&N configuration

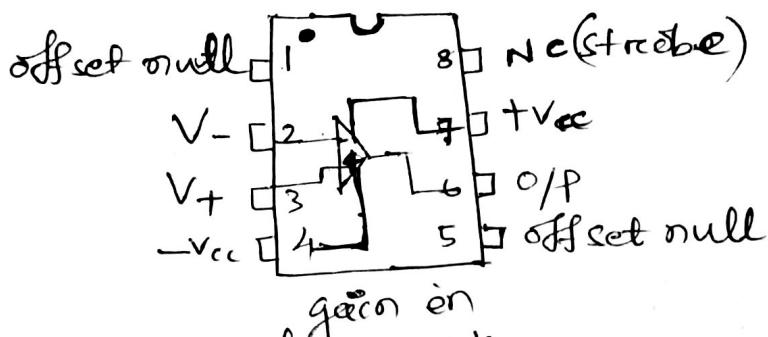


→ 4 Types of OPAMP's

- 1) voltage gain — voltage in and voltage out
- 2) current gain — current in and current out.
- 3) Transconductance — voltage in and current out.
- 4) Trans-resistance — current in and voltage out.

→ The output of OPAMP should be zero, when the voltage difference between the inputs is zero.

→ But in most of OP-amps, the output will not be zero, when off, hence there will be a minute voltage from it.

OPAMP - Amplification

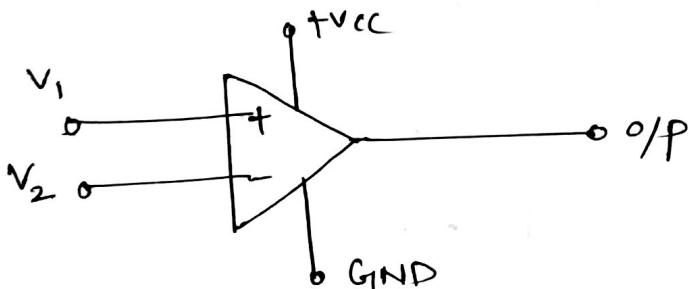

→ The amplified output signal from the output Amp is the difference between the two input signals.

If both the inputs are supplied with the same voltage, the OP-Amp will then take the difference between the two voltages and it will be zero.

→ The OP-Amp will then take the difference between the two voltages and it will be zero.


$$\rightarrow A_v = \frac{V_o}{V_i} = \frac{\text{---}}{\Delta V_i} \quad \text{with } \frac{V_o}{D} = n$$

→ The OP-Amp will multiply ~~the~~ its gain 1,000000
 So the output voltage is zero

18


When 2 volts is given to one input, and 1 volt in the other, then the op-Amp will take its difference and multiply with gain. That is also yield $1 \text{V}_\text{OH} \times 2,000,000$, But often gain is also very high.

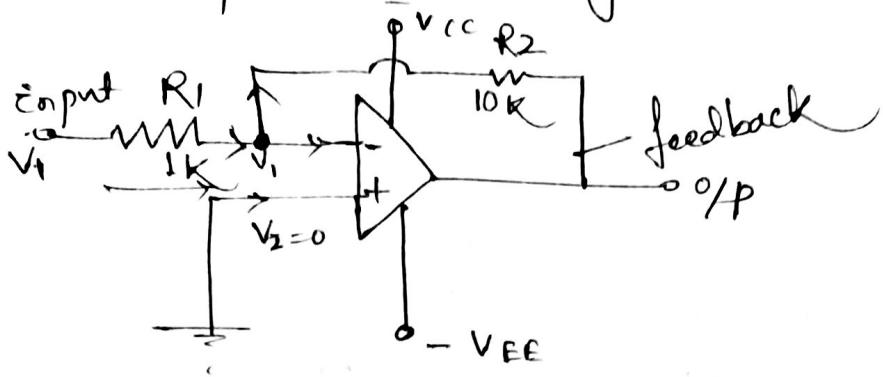→ So to reduce the gain, feedback from the output to the input is usually done through a resistor.



Inverting Amplifier :

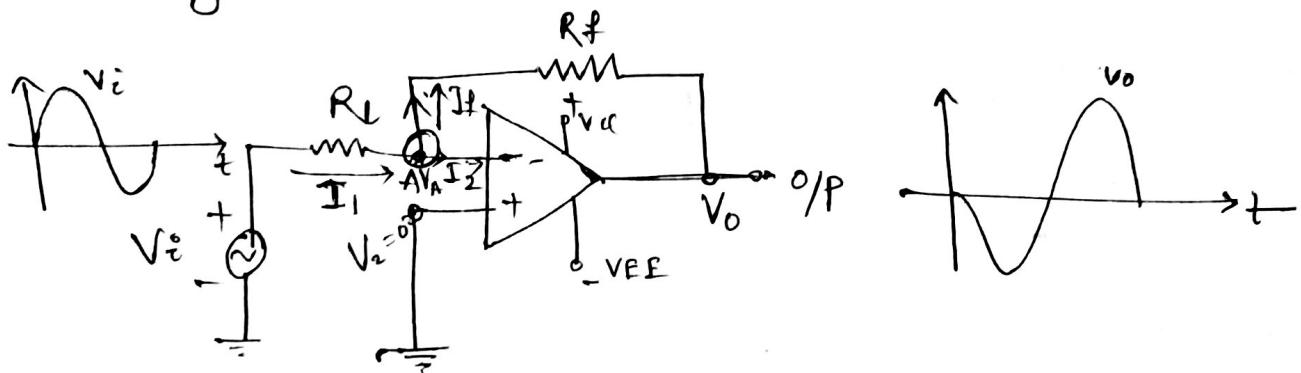An op-Amp circuit that produces an amplified output signal that is 180° out of phase with the input signal.



Applying KCL at node A

$$I_1 = I_F + I_2 \quad \left. \right\} \quad \because V_A = 0 \text{ virtual}$$

$$\Rightarrow I_1 = I_F$$

$$\Rightarrow \frac{V_0 - V_A}{R_1} = \frac{V_A - V_O}{R_f} \quad \text{--- (1)}$$

$$\left. \right\} \text{In ideal op-amp } V_1 = V_2 \\ V_1 = 0, \Rightarrow V_1 = V_2 = 0 = V_A$$

(1)

$$\frac{V_i - 0}{R_1} = \frac{0 - V_o}{R_f}$$

$$\Rightarrow V_o = -\frac{R_f}{R_1} \cdot V_i$$


$$\Rightarrow \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

$$= A_v = \text{voltage gain} = \frac{V_o}{V_i}$$

$$\Rightarrow A_v = -\frac{R_f}{R_1}$$

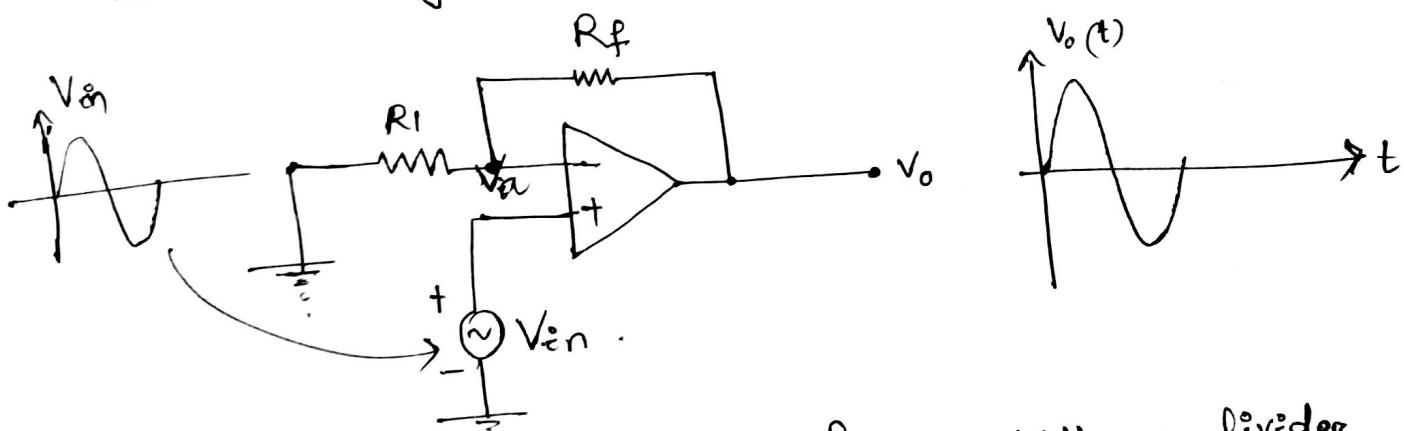(2) Non-Inverting Amplifier

A non-inverting amplifier is an op-amp circuit designed to provide positive gain. The output is directly applied to the non-inverting terminal.



→ The Resistors R_f and R_1 form a Voltage divider

$$\Rightarrow V_a = \frac{V_o \times R_1}{R_1 + R_f}$$

From concept of virtual ground -

$$V_{en} = V_a$$


$$\Rightarrow V_{en} = \frac{V_o \times R_1}{R_1 + R_f} \Rightarrow V_o = \frac{V_{en} (R_1 + R_f)}{R_1}$$

$$\rightarrow V_o = \left(1 + \frac{R_f}{R_i}\right) V_{in}$$

$$\Rightarrow \frac{V_o}{V_{in}} = \boxed{A_v = 1 + \frac{R_f}{R_i}}$$

~~2m~~ Application of Non-inverting Amplifier as
Voltage follower

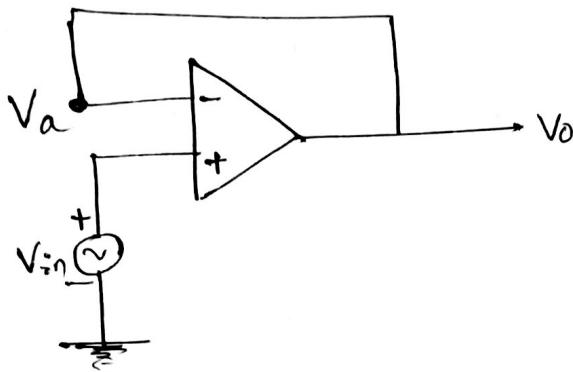A voltage follower is an OP-Amp circuit in which output follows the input. It is also called as unity gain Buffer amplifier.



due to physical short circuit

$$\rightarrow V_a = V_o$$

due to Virtual ~~ground~~ ground concept

$$V_a = V_{in}$$

$$\Rightarrow V_{in} = V_o$$

$$\Rightarrow A_v = \frac{V_o}{V_{in}} = 1$$

It is used as buffer

It is also used in instrumentation amplifier.