
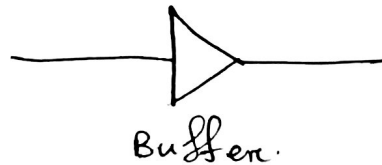


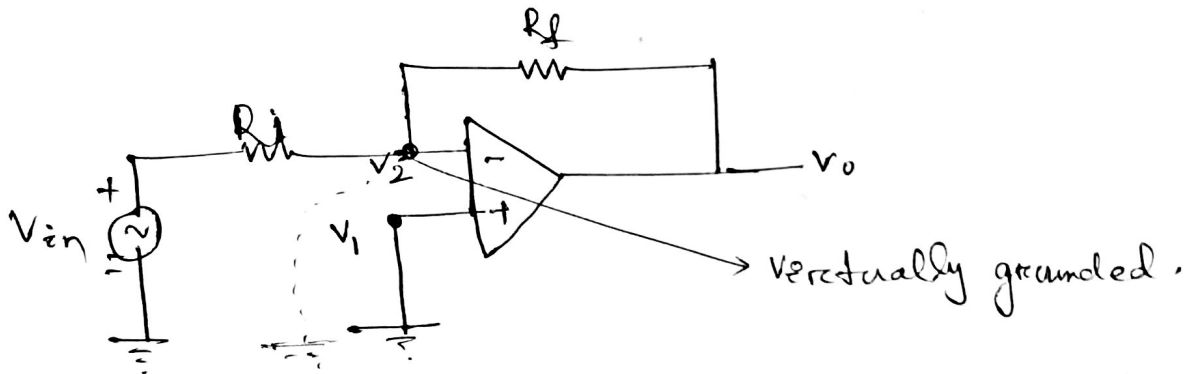→ Since Buffer has high input impedance and low output impedance.



Concept of Virtual ground



→ A point in any circuit is said to be grounded if the potential at that point is equal to the ground Potential.

0-volt.

$$V_o = A_{OL} (V_1 - V_2)$$

$$(V_1 - V_2) = \frac{V_o}{A_{OL}}$$

For ideal op-Amp

$$A_{OL} \rightarrow \infty$$

$$V_1 - V_2 = \frac{V_o}{\infty} = 0$$

$$\Rightarrow \boxed{V_1 = V_2}$$

∴ Since $V_1 = 0$ (directly ground)


$\Rightarrow V_2 = 0$ (virtually ground.)

OP-AMP - As a differentiator :-

or,
OP-Amp as a differential amplifier :-

→ A circuit that perform mathematical differentiation of input signal is called differentiator.

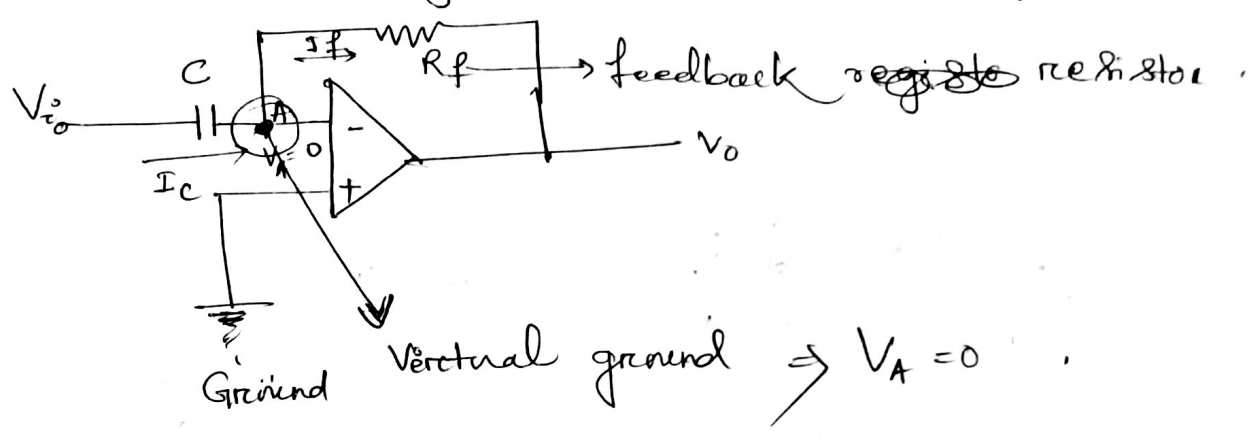→ The output of a differentiator is proportional to the rate of change of its input signal.



Now applying KCL at node A

$$I_c = I_f$$

$\left\{ \begin{array}{l} I_c = \text{current flowing} \\ \text{through the capacitor.} \end{array} \right.$

$$\Rightarrow C \cdot \frac{dV_c}{dt} = \frac{V_A - V_o}{R_f}$$


$$\Rightarrow C \cdot \frac{d(V_i)}{dt} = \frac{-V_o}{R_f}$$

$$\Rightarrow \frac{d(V_i)}{dt} = \frac{-V_o}{R_f C}$$

$$\Rightarrow \boxed{V_o = -R_f C \cdot \frac{dV_i}{dt}}$$


$$\boxed{V_c = V_i}$$

$V_o = \text{output signal.}$

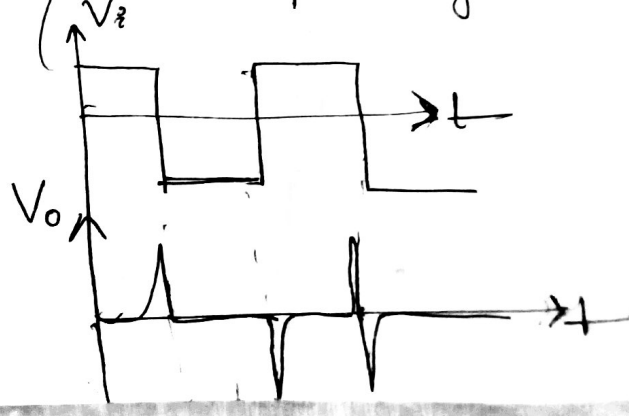

OP-AMP - As integrator

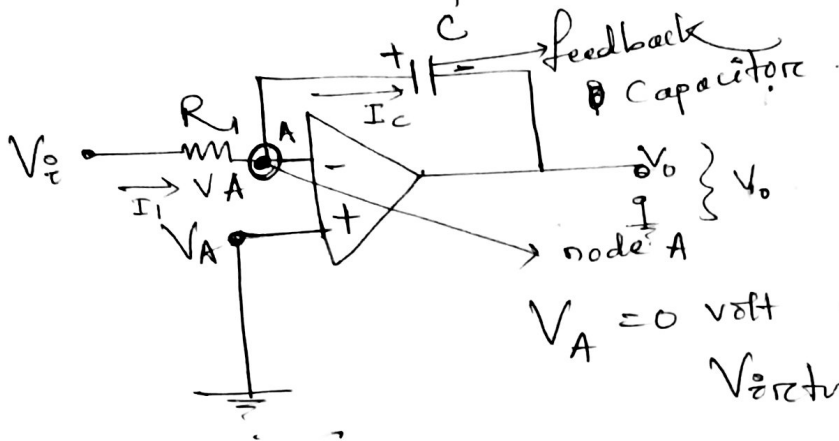- A circuit that performs integration of input signals is called an integrator.
- The output of an integrator is proportional to the Area of the input waveform over a period of time



$V_A = 0$ volt due to ~~virtual~~ Virtual ground concept

Applying KCL at node (A)

$$I_1 = I_c$$

$$\frac{V_i - V_A}{R_1} = \frac{V_o - V_A}{C} \cdot \frac{dV_o}{dt} \quad \left(\because I_c = C \frac{dV}{dt} \right)$$

$$\Rightarrow \frac{V_i}{R_1} = C \cdot \frac{dV_o}{dt}$$



$$\Rightarrow \frac{V_i}{R_1} = C \cdot \frac{d(-V_o)}{dt}$$

Now integrating both side

$$\Rightarrow \int_0^t \frac{V_i}{R_1} dt = -C \int_0^t \frac{dV_o}{dt} dt$$


$$\Rightarrow \frac{1}{R_1} \int_0^t V_i dt = -C \cdot V_o$$
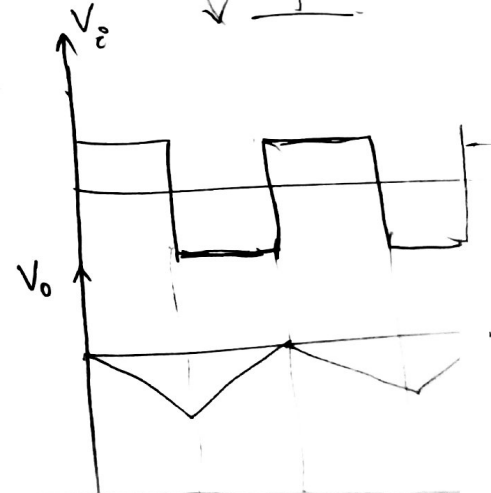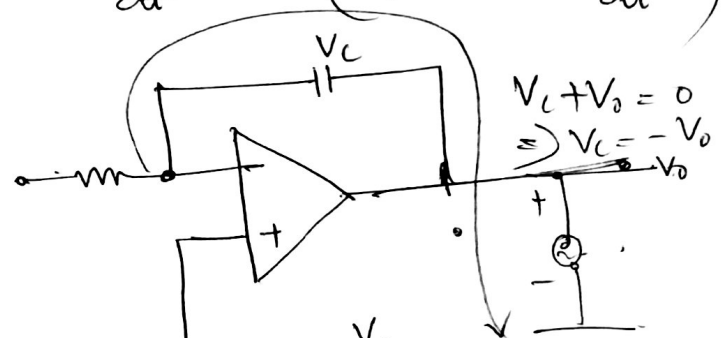
$$\Rightarrow V_o = -\frac{1}{RC} \int_0^t V_i dt$$



OP-AMP as Summing Amplifier:-

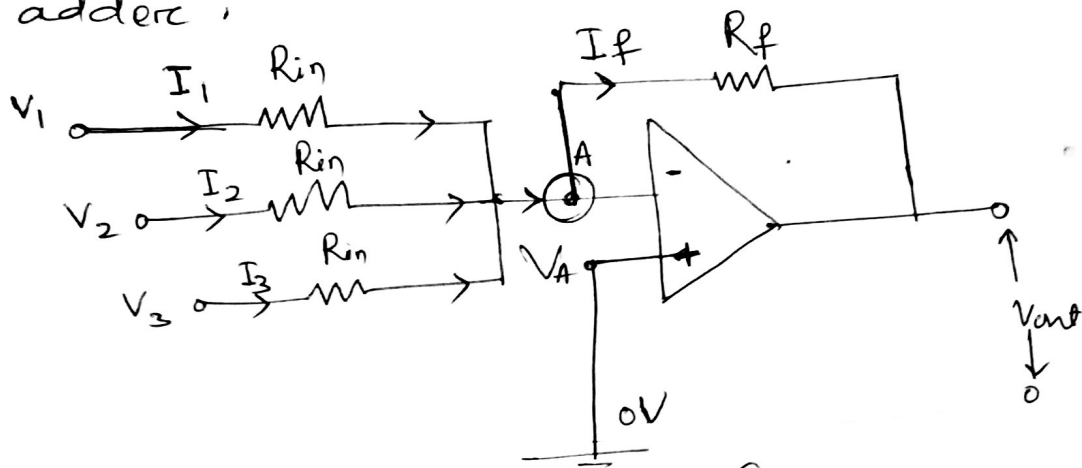A Summing amplifier is an operational amplifier circuit which combines ~~the~~ two or more ^{i/p} voltages into a single output voltage. It is also called voltage adder.



At Node **(A)** ~~Inverting~~ (Inverting Summing Amplifier)

$$I_F = I_1 + I_2 + I_3 \Rightarrow - \left[\frac{V_1}{R_{in}} + \frac{V_2}{R_{in}} + \frac{V_3}{R_{in}} \right]$$

As we know that from inverting amplifier

$$V_o = - \left(\frac{R_f}{R_{in}} \right) V_{in}$$


$$\Rightarrow V_o = - \left[\frac{R_f}{R_{in}} V_1 + \frac{R_f}{R_{in}} V_2 + \frac{R_f}{R_{in}} V_3 \right]$$

$$\Rightarrow V_{out} = - \frac{R_f}{R_i} [V_1 + V_2 + V_3]$$

$$\Rightarrow V_{out} = - \frac{R_f}{R_i} [V_1 + V_2 + V_3 \dots] \text{ for multiple number of input signal.}$$

Problem on Summing amplifier

Ex-1

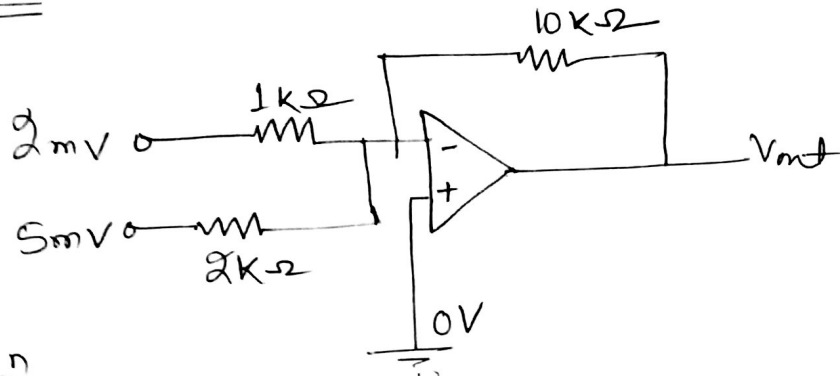

Solⁿ

$$V_{out} = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right)$$

$$\Rightarrow V_{out} = - \left[\frac{10 \text{ k}\Omega}{1 \text{ k}\Omega} \times 2 \text{ mV} + \frac{10 \text{ k}\Omega}{2 \text{ k}\Omega} \times 5 \text{ mV} \right]$$

$$\Rightarrow V_{out} = - [20 \text{ mV} + 25 \text{ mV}]$$


$$\Rightarrow \boxed{V_{out} = -45 \text{ mV}}$$

- Sign ~~ind~~ indicates it is an inverting amplifier.

2mp L.O

(16)

Non-inverting Summing Amplifier

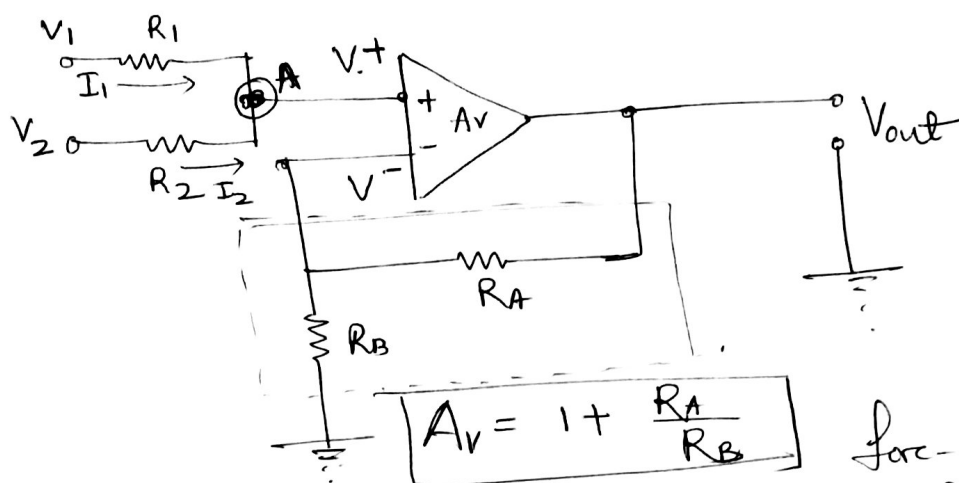

for Non-inverting Amplifier gain

$A_v = \text{voltage gain}$

at Node (A) applying KCL

$$I_{R_1} + I_{R_2} = 0$$

$$\frac{V_1 - V^+}{R_1} + \frac{V_2 - V^+}{R_2} = 0$$

$$\Rightarrow \frac{V_1}{R_1} - \frac{V^+}{R_1} + \frac{V_2}{R_2} - \frac{V^+}{R_2} = 0$$

$$\text{Let } R_1 = R_2 = R$$

$$\Rightarrow \frac{V_1 + V_2}{R} - \frac{2V^+}{R} = 0 \Rightarrow \frac{V_1 + V_2}{R} = \frac{2V^+}{R}$$


$$\Rightarrow \boxed{V^+ = \frac{V_1 + V_2}{2}}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{V_{out}}{V^+} = \left(1 + \frac{R_A}{R_B}\right)$$

$$\text{Let } R_A = R_B = R \Rightarrow V_{out} = \left(1 + \frac{R_A}{R_B}\right) \times V^+ \\ \Rightarrow V_{out} = 2 \times \frac{V_1 + V_2}{2} = V_1 + V_2$$

OP-AMP as Subtractor

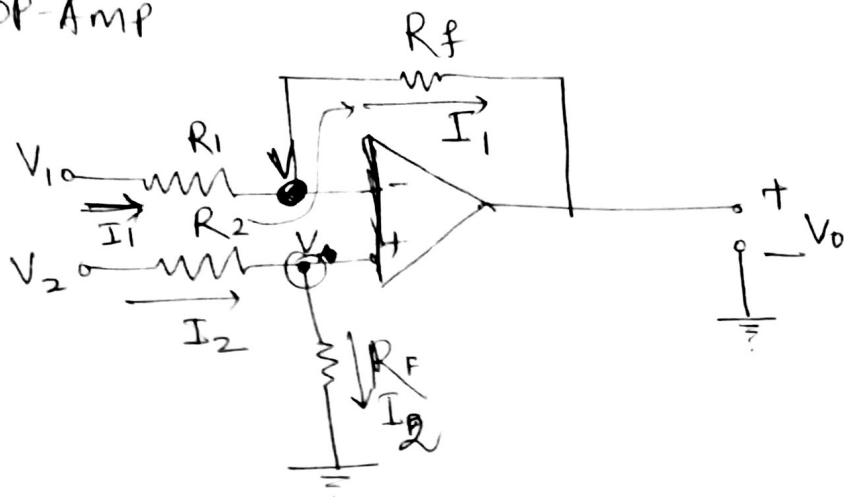The subtraction of two input voltages is done by the OP-AMP



Let us consider a non-inverting amplifier.

$$\Rightarrow I_2 = \frac{V_2 - V}{R_2} = \frac{V - 0}{R_f}$$

$$\Rightarrow I_2 = \frac{V_2}{R_2} - \frac{V}{R_2} = \frac{V}{R_f}$$

$$\Rightarrow \frac{V_2}{R_2} = \frac{V}{R_f} + \frac{V}{R_2} \Rightarrow \frac{V_2}{R_2} = V \left[\frac{R_2 + R_f}{R_2 R_f} \right]$$

$$\Rightarrow V = V_2 \left[\frac{R_f}{R_2 + R_f} \right] \quad \text{--- (A)}$$

Similarly

$$\begin{aligned} I_1 &= \frac{V_1 - V}{R_1} = \frac{V - V_0}{R_f} \\ &= \frac{V_1}{R_1} - \frac{V}{R_1} = \frac{V}{R_f} - \frac{V_0}{R_f} \end{aligned}$$

$$\Rightarrow \frac{V_0}{R_f} = \frac{V}{R_f} + \frac{V}{R_1} - \frac{V_1}{R_1}$$

$$\Rightarrow \frac{V_0}{R_f} = V \left[\frac{R_f + R_1}{R_f R_1} \right] - \frac{V_1}{R_1}$$

\Rightarrow Now putting 'V' from equation (1) we get

$$\Rightarrow \frac{V_0}{R_f} = V_2 \left(\frac{R_f}{R_f + R_2} \right) \left[\frac{R_f + R_1}{R_f R_1} \right] - \frac{V_1}{R_1}$$

$$\Rightarrow V_0 = V_2 \left(\frac{R_f}{R_f + R_2} \right) \left[\frac{R_f + R_1}{R_1} \right] - \frac{R_f V_1}{R_1}$$

$$\text{if } R_1 = R_2$$


$$V_0 = \frac{R_f}{R_1} [V_2 - V_1]$$

$$\text{if } R_f = R_1 = R_2 = R$$

$$\Rightarrow \boxed{V_0 = V_2 - V_1}$$

Differential amplifier (when both i/p's are given)

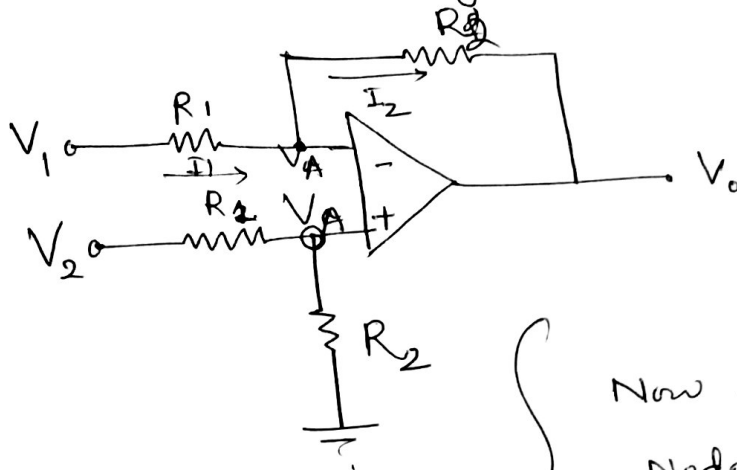A circuit that amplifies the difference between the two input signals.



By voltage division

$$V_A = \frac{R_2 \times V_2}{R_1 + R_2} \quad (1)$$

Now applying KCL at Node - A

$$I_1 = I_2$$

$$\frac{V_1 - V_A}{R_1} = \frac{V_A - V_0}{R_2}$$

$$\Rightarrow \frac{V_1}{R_1} - \frac{V_A}{R_1} = \frac{V_A}{R_2} - \frac{V_0}{R_2}$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_0}{R_2} = \frac{V_A}{R_1} + \frac{V_A}{R_2}$$

$$\Rightarrow \frac{V_0}{R_2} = \frac{V_A}{R_2} + \frac{V_A}{R_1} - \frac{V_1}{R_1}$$

$$\frac{V_0}{R_2} = V_A \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_1}{R_1}$$

$$\Rightarrow V_0 = V_A \left(1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} V_1 \quad (2)$$

Now putting V_A from above equation (1) in (2)

$$\Rightarrow V_0 = \frac{R_2 \times V_2}{R_1 + R_2} \left(\frac{1 + \frac{R_2}{R_1}}{1} \right) - \left(\frac{R_2}{R_1} \right) V_1$$

20

$$\Rightarrow V_0 = \frac{R_2}{R_1} V_2 - \frac{R_2}{R_1} V_1$$

$$\Rightarrow \boxed{V_0 = \frac{R_2}{R_1} (V_2 - V_1)}$$

$$\Rightarrow \boxed{V_0 = \frac{R_2}{R_1} (V_2 - V_1)}$$